



WEEK-5 PRESENTATION ANALOG DESIGN INTERNSHIP

Mentor

Dr G S Javed

Technical Lead @Intel

Co-Mentor

Dr Naushad Alam

Professor

Prepared By:

Munazir Reza

B.Tech (Electronics engg.)

Z.H.C.E.T, A.M.U, Aligarh

SESSION OUTLINE

- Previous Preview
- ADT Toolbox
- Source Follower Amplifier design
- Common Source Amplifier design
- Differential Pair design
- Operational Amplifier design
- Project: Two stage op-amp design



WEEK-1

- Extract Charts for NMOS & PMOS
- g_m/g_{ds} vs g_m/i_d
- V_{gs} vs g_m/i_d
- I_d/w vs g_m/i_d
- Design Common Source and Source Follower Amplifier from charts.
- Observe large (W/L) ratios.



Week-2

- Design Current Mirror
- Design Delay Cell
- Design Common Source amplifier, Differential Pair and op-amp with Small (W/L) ratios.

Week-3

- Design Cascode CS amplifier & op-amp.



ADT TOOLBOX

- Official link: <https://at.master-micro.com>

The screenshot shows the homepage of the ADT Toolbox website. The header features the ADT logo (Analog Designer's Toolbox) and navigation links: 'What is ADT?', 'ADT Features', 'Pricing Plans', 'Contact Us', 'Downloads', 'Request Demo' (a grey button), and 'Dashboard' (a blue button). The main content area has the title 'Analog Designer's Toolbox' in large white text, followed by the tagline 'From Designers...To Designers'. Below this are two buttons: a red 'Watch ADT Demo' button and a blue 'Download Windows Version v1.8' button. A link 'Not your OS?' is positioned below the blue button. To the right, there is a stack of three overlapping screenshots of the software interface, showing various plots and data tables. On the far right edge, there is a vertical social media sidebar with icons for LinkedIn, Facebook, and YouTube.

DESIGN BY USING ADT TOOLBOX

- The Analog Designer's Toolbox (ADT): Towards a new paradigm for analog IC design.
- ADT provides a turnkey solution that enables everyone to reap the benefits of the GM/ID design methodology powered by pre-computed lookup tables (LUTs).
- At the device level, ADT Device Xplore gives an easy interface to plot arbitrary design charts involving complex expressions.
- The designer can explore devices from different technologies at different corners and temperatures, and extract simulator-accurate design points while taking second-order effects into consideration.

CONTINUE.....

- At the block level, ADT Design Xplore gives the designer the power of design space exploration, constraints management, live tuning, and optimization, all in a single cockpit without invoking the simulator.
- Moreover, with a single click, ADT can build the testbenches in the background and report the results from your favorite simulator. The aim of ADT is to boost productivity, restore designer's intuition, and make the design process systematic, optimized, and fun!



ADT TOOLBOX INTERFACE

LUT GENERATION

Analog Designer's Toolbox (Non-commercial use only)

File View Tabs Tools Help

Work Directory: C:\Users\ASUS\Desktop\ADT_Windows_Release_v1.1.8\ADT_Windows_Release_v1.1.8\ADT

LUT Generation

Simulator Settings

Simulator: LTspice
Simulation Command: C:\Program Files\TC\LTspiceXVII\XVIIx64.exe
Netlist Path: Release_v1.1.8\ADT\ltspice_example\ex_ltspice_netlist.cir

LUT Save Settings


Save Path: If left empty, the LUTs will be saved in the work directory.
LUT Prefix Name: ex
☐ Save every device corner in a separate LUT file.

Device Characterization Parameters

MOSFET BJT


Ref. Width per Finger: 10u
Ref. No. of Fingers: 1
Length: 0.18u:0.02u:0.5u, 0.6u:0.1u:1u, 1.2u:0.2u:2u
VGS: 0:20m:1.2, 1.25:50m:1.8
VDS: 25m:25m:1.2, 1.3:0.1:1.8
VSB: 0:50m:1.2, 1.3:0.1:1.8
Output Variables: 0:1 0:2 0:3 0:999 1000 1001 1002 2196 2

ADT: DEVICE XPLORE

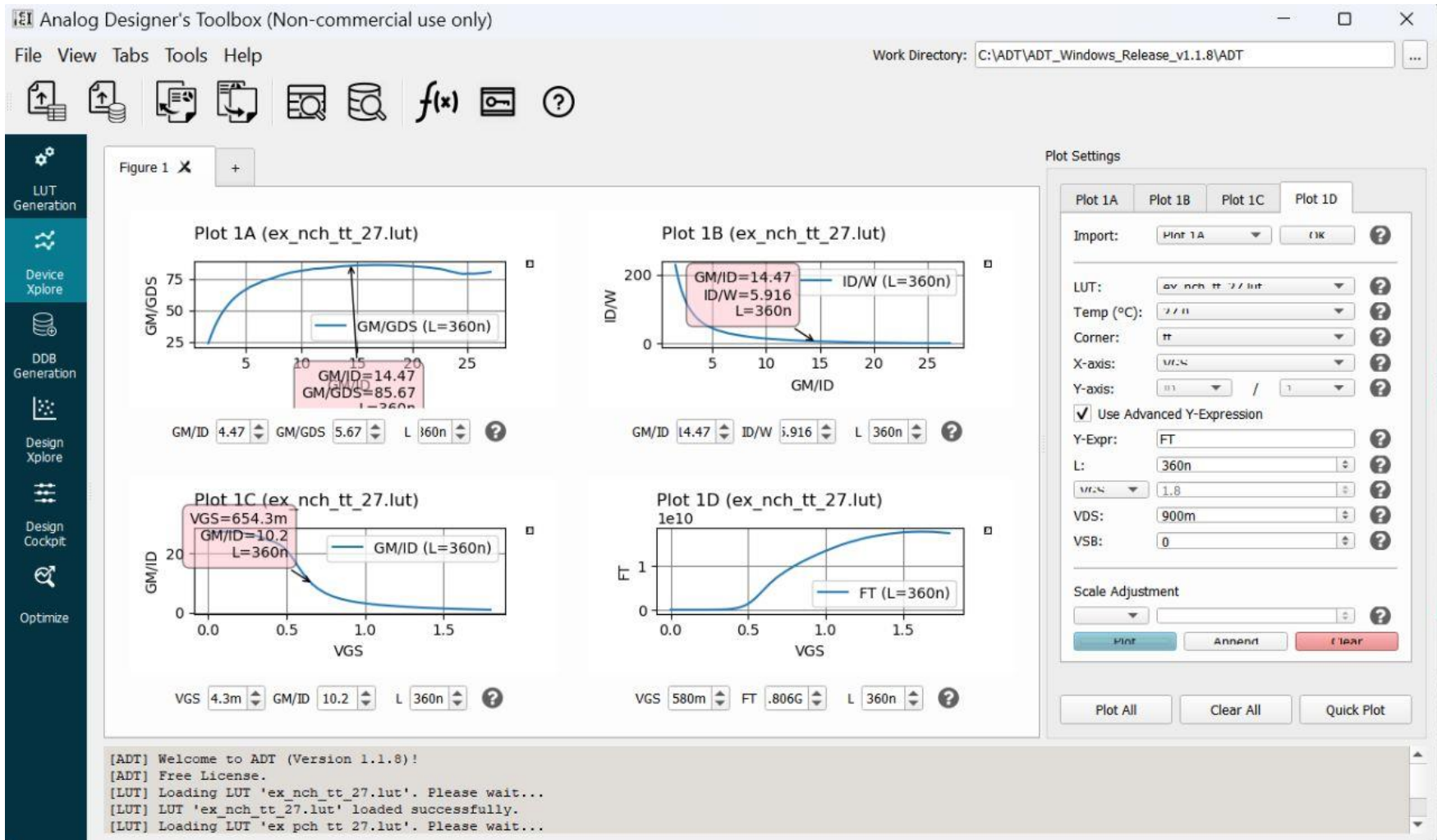


LUT INTERFACE

GM/GDS VS GM/ID CHART

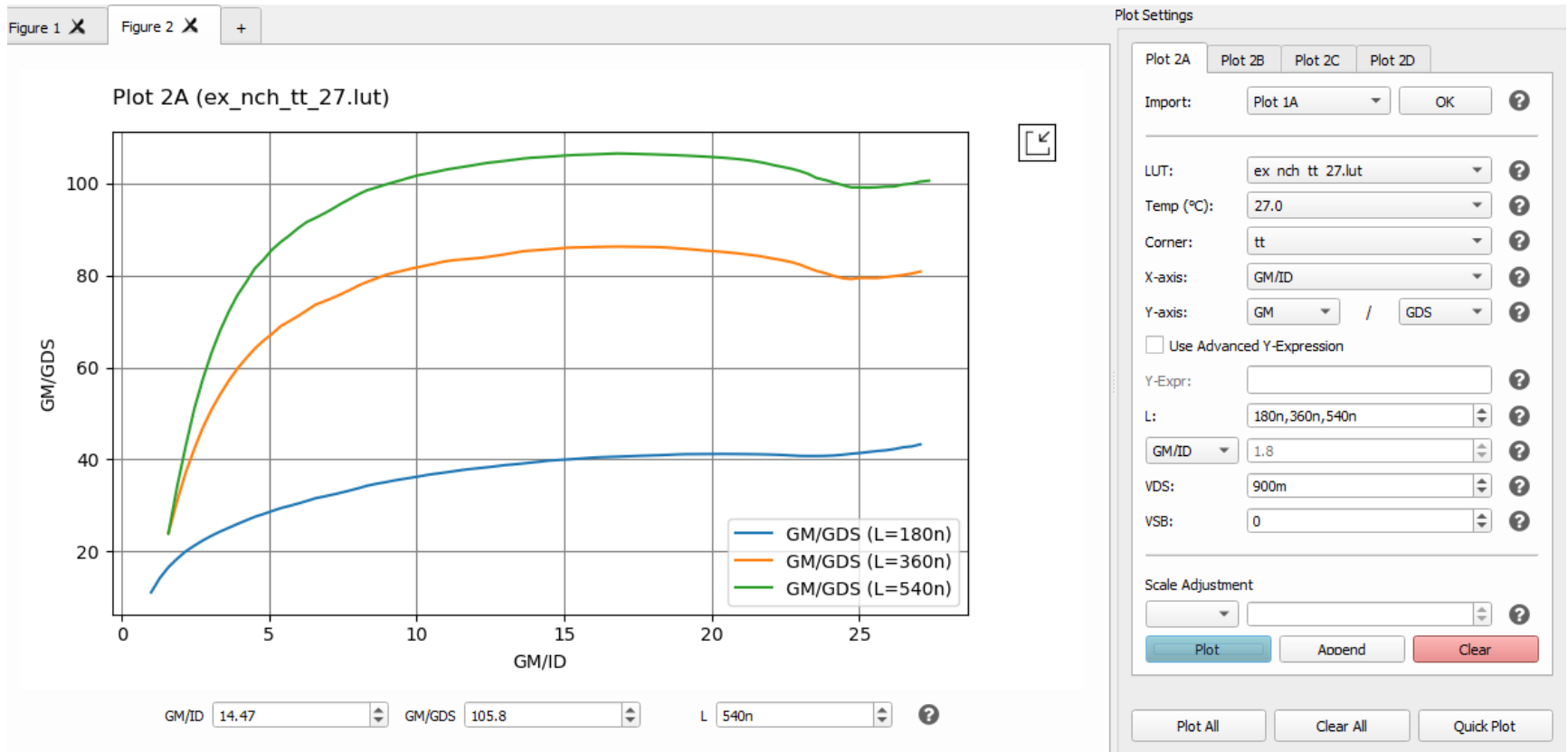

ID/W VS GM/ID CHART

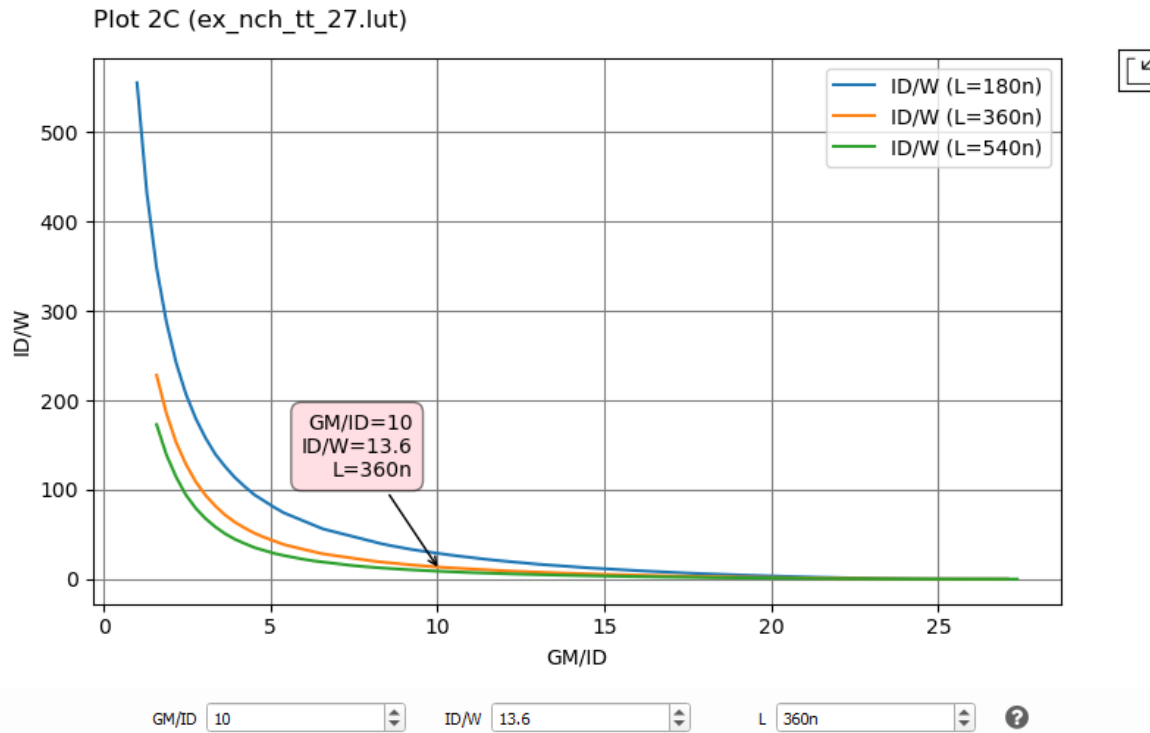

Plot 2A Plot 2B Plot 2C Plot 2D

Import: Plot 1A OK ?

LUT: ex_nch_tt_27.lut ?

Temp (°C): 27.0 ?

Corner: tt ?

X-axis: GM/ID ?

Y-axis: ID / W ?

☐ Use Advanced Y-Expression

Y-Expr: ?

L: 180n,360n,540n ?

GM/ID: 10 ?

VDS: 900m ?


VSB: 0 ?

Scale Adjustment

Plot Append Clear

Plot All Clear All Quick Plot

VGS VS GM/ID CHARTS

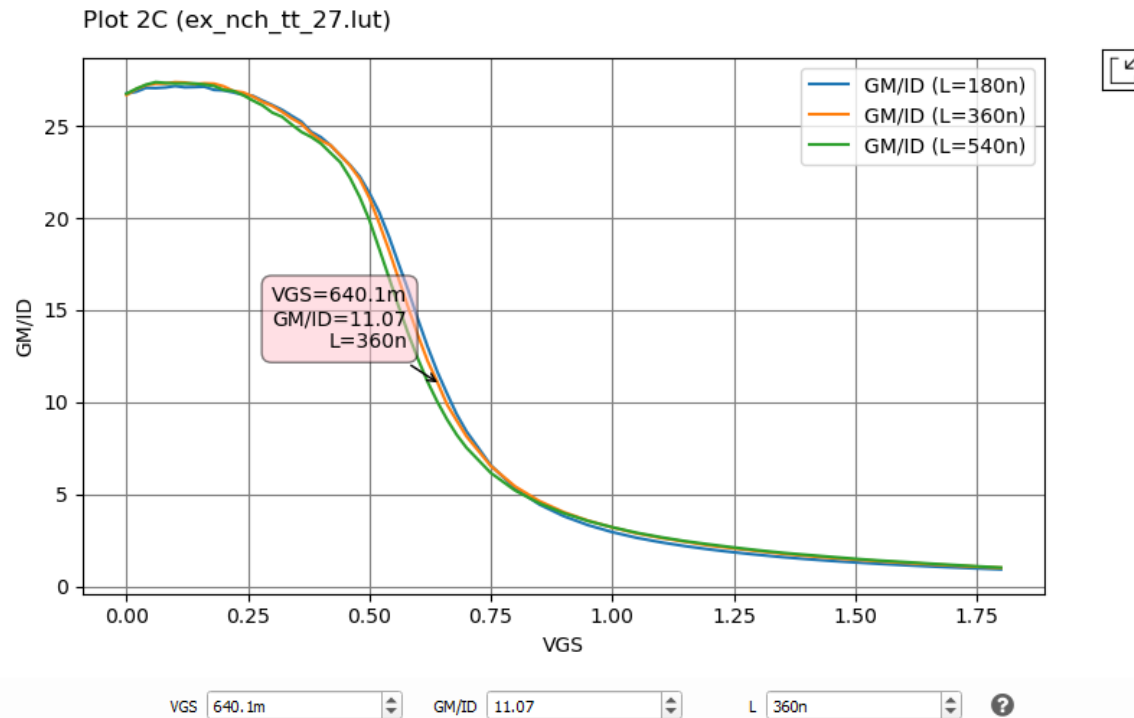

Plot 2A Plot 2B Plot 2C Plot 2D

Import: Plot 1A OK ?

LUT: ex_nch_tt_27.lut ?

Temp (°C): 27.0 ?

Corner: tt ?

X-axis: VGS ?

Y-axis: GM / ID ?

☐ Use Advanced Y-Expression

Y-Expr: ?

L: 180n,360n,540n ?

VGS: 1.8 ?

VDS: 900m ?

VSB: 0 ?

Scale Adjustment

Plot Append Clear

Plot All Clear All Quick Plot

Note: We can draw many charts from ADT Device Xplore
e.g: ID/GDS, GBW, FT vs GM/ID



MODEL FILE USED

- File: CMOS180.txt
- Supply Voltage: 1.8 V
- <https://web.stanford.edu/~murmnn/gmid>
- 0.18 μ m CMOS models



SOURCE FOLLOWER AMPLIFIER

- **Specs:**

- $A_v=1$ $CL= 1\text{pF}$

- $R_{out}=75\ \Omega$

- $g_m/i_d= 10 \dots(\text{Choose})$

- $g_m/g_{ds}=76.93$

$I_d/w=14.58$

$V_{gs}=870\text{mV}$

- $g_m=13.33\ \text{mS}$

$W1=91.22\ \mu\text{m}$

$V_{in}=1.77\text{V}$

- $I_d=1.33\ \text{mA}$

$W1=66.6\ \mu\text{m}$ (tuning to get R_{out})

- $g_{ds}=172.2\ \mu\text{S}$

- $R_{o1}=5.77\ \text{K}\Omega$

- Let $R_{o2}=10\ \text{K}\Omega$

$g_{ds}=100\ \mu\text{S}$


- $I_d/g_{ds}=13.3$

- $g_m/i_d=5.112$

$g_m/g_{ds}=67.36$

$V_{gs}=819.2\text{mV}$


- $W2=31\ \mu\text{m}$

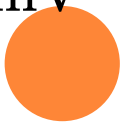

SIMULATION

```
.include "C:\Users\ASUS\Desktop\CMOS180.txt"
```
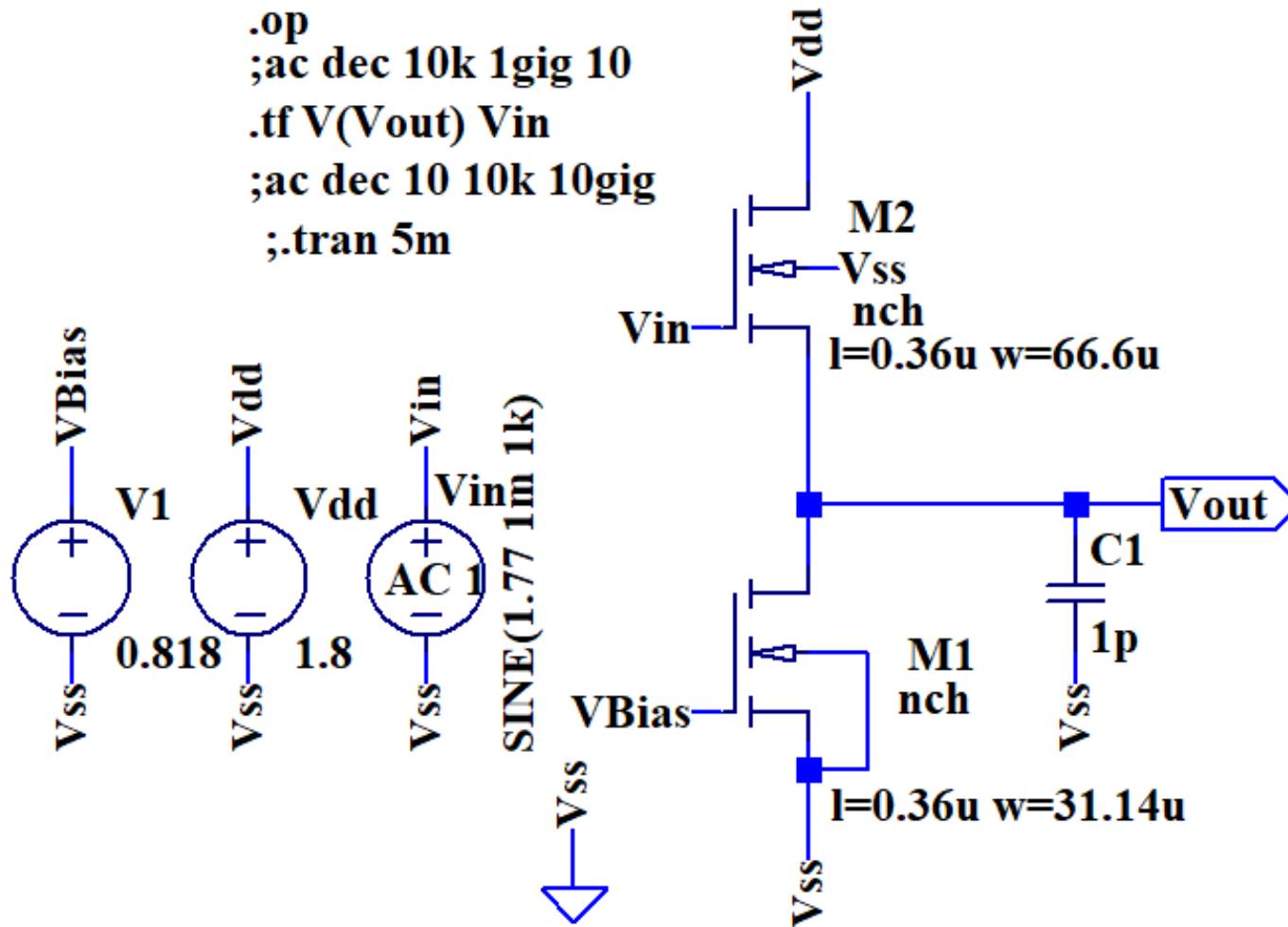
```
.op  
;ac dec 10k 1gig 10  
.tf V(Vout) Vin  
;ac dec 10 10k 10gig  
;.tran 5m
```




RESULT

Simulated Value	Specifications
$A_v = 0.814 \text{ v/v}$	$A_v = 1 \text{ v/v}$
$BW = 1.82 \text{ GHz}$	$BW = 2.12 \text{ GHz}$
$R_{out} = 75.1 \text{ } \Omega$	$R_{out} = 75 \text{ } \Omega$
$I_d = 1.3 \text{ mA}$	$I_d = 1.33 \text{ mA}$
$V_{out(dc)} = 0.87 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$



TRANSIENT ANALYSIS

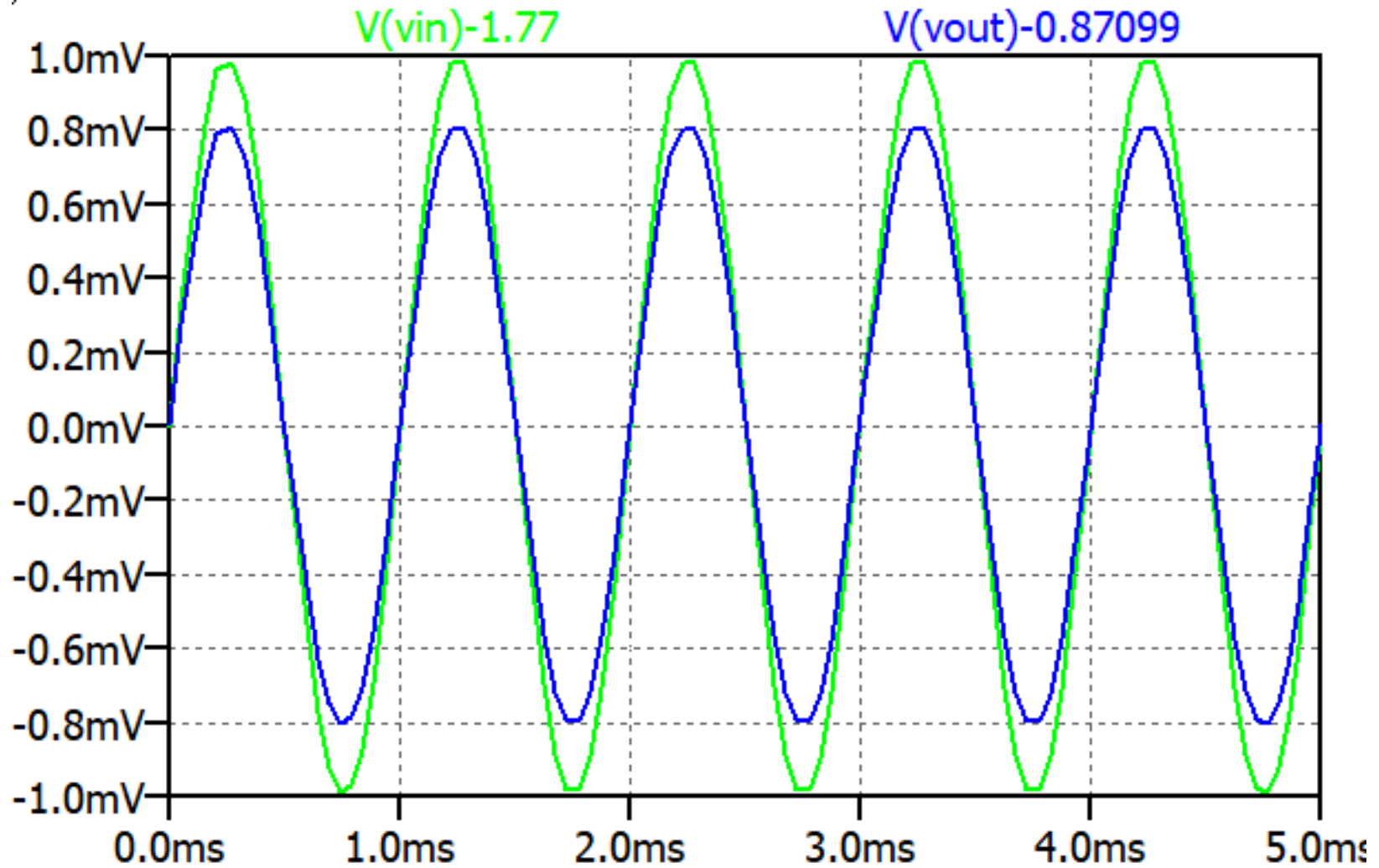


$V_{in}(p-p)=2 \text{ mV}$

$V_{out}=1.6 \text{ mV}$

Gain=0.8



FREQUENCY RESPONSE

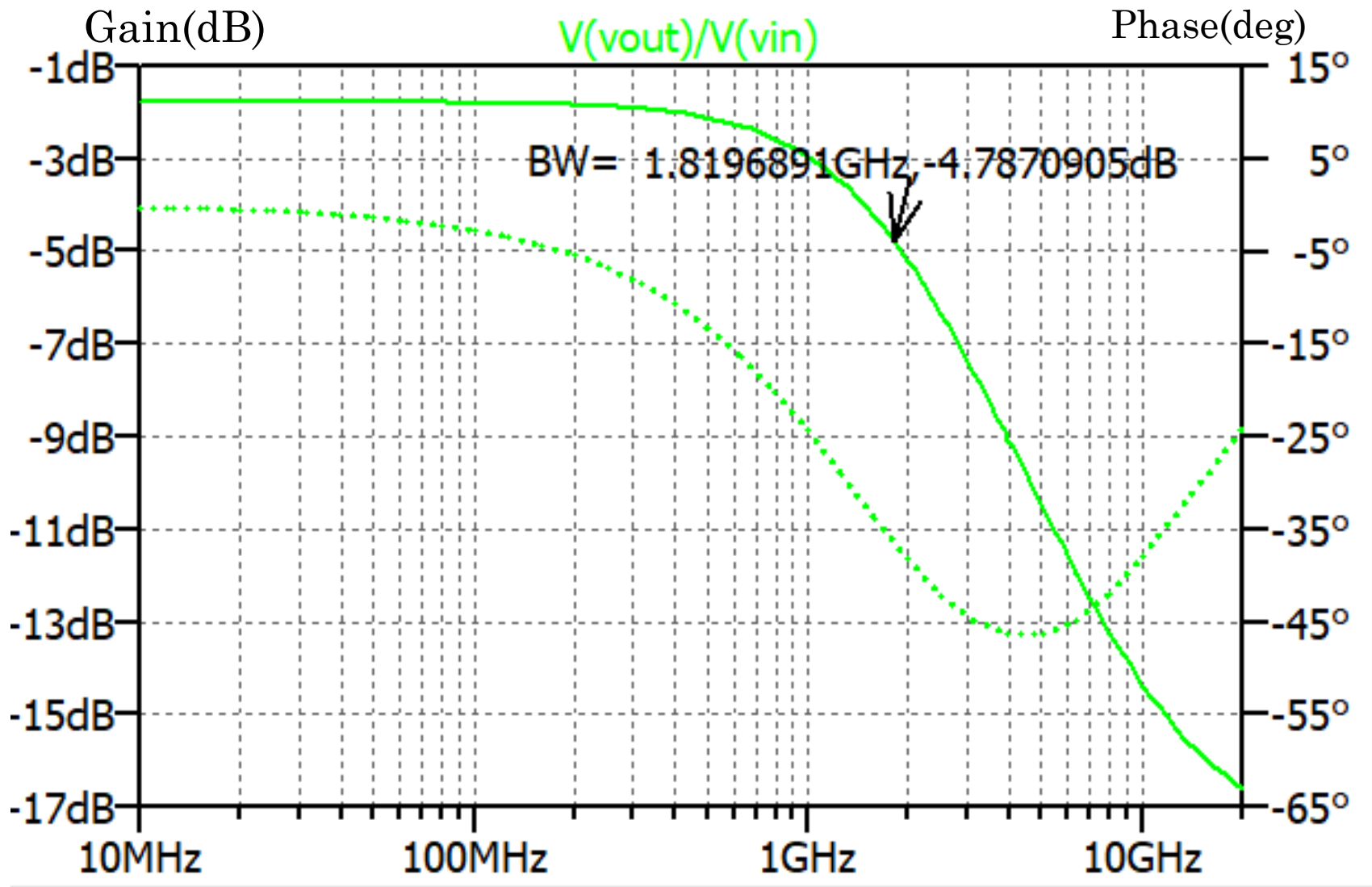

Frequency

COMMON SOURCE AMPLIFIER

Specification:

Gain(A_v)=40

R_{out} =150 K Ω

BW=25 MHz

Calculation:

Formula Used

- $BW(3dB \text{ freq}) = \frac{1}{2\pi \cdot R_{out} \cdot C_L}$ $A_v = g_m \cdot R_{out}$
- $R_{out} = r_{o1} // r_{o2}$
- $C_L = 42.44 \text{ fF}$
- $g_m / I_D = 10$ (Choose)
- $g_m = 0.266 \text{ mS}$
- $I_D = 26.6 \mu A$
- $g_m / g_{ds} = 81.72$ from chart $I_D / W = 13.6$
- $g_{ds} = 3.25 \mu S$ $W_1 = 1.95 \mu m$
- $R_{o1} = 307.21 \text{ K}\Omega$ $V_{gs1} = 657.8 \text{ mV}$




Continue....

- $R_{o2}=293.12 \text{ K } \Omega$
- $g_{ds2}=3.41 \text{ } \mu\text{S}$
- $(I_d/g_{ds})_2=7.8$
- $(g_m/i_d)_2= 7.106 \text{ from chart}$
- $(I_d/w)_2=7.312 \text{ from chart}$
- $V_{gs2}=712.9 \text{ mV}$
- $W_2= 3.63 \text{ } \mu\text{m}$



SIMULATION
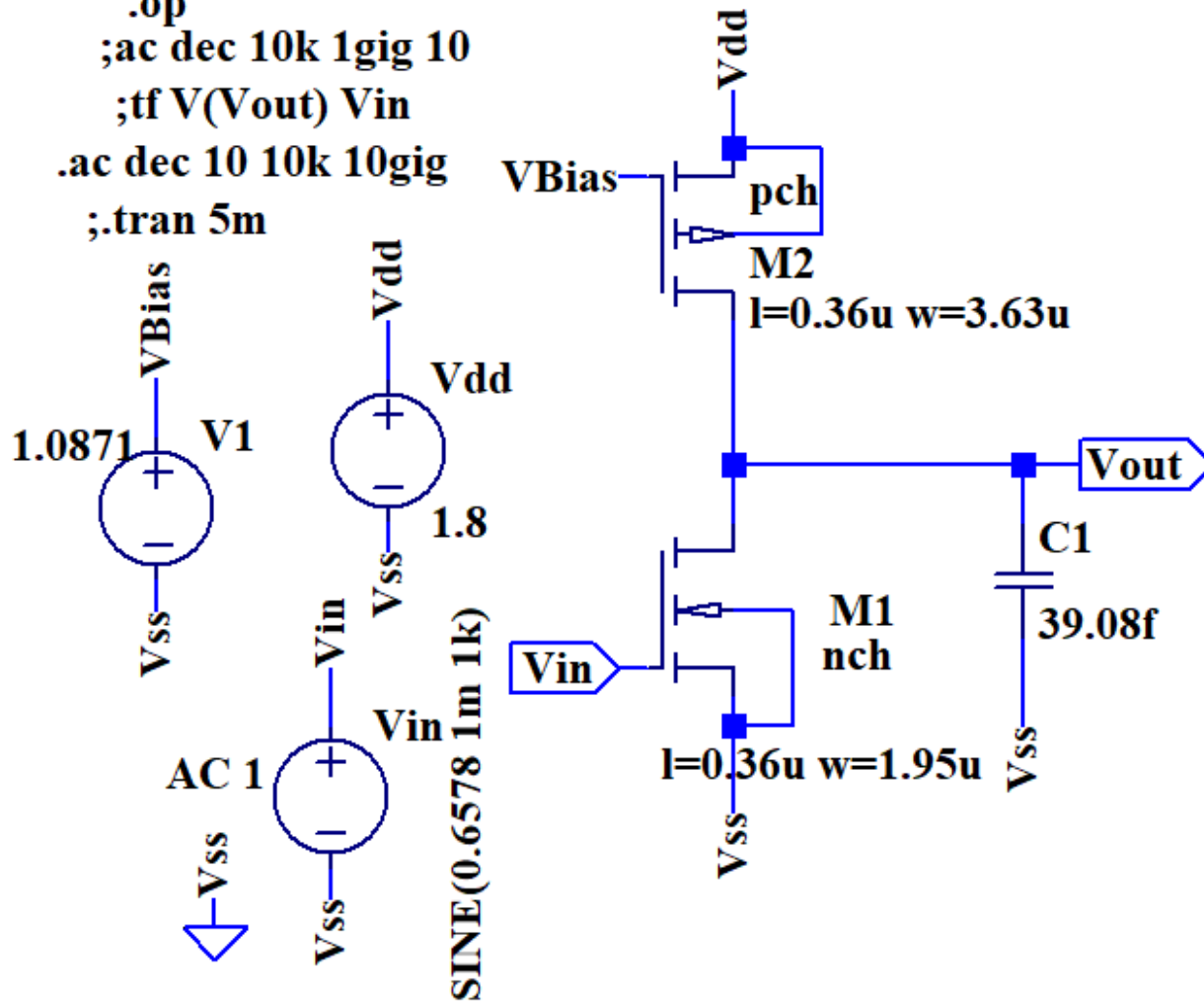
```
.include C:\Users\ASUS\Desktop\CMOS180.txt
.op
;ac dec 10k 1gig 10
;tf V(Vout) Vin
.ac dec 10 10k 10gig
;.tran 5m
```



SOME CHANGES

Internal capacitance at node $V_{out} = c_{gd2} + c_{gd1}(1+A_v)$

$$C(V_{out}) = 3.36 \text{ fF}$$

$$\text{So } C_L = 42.44 \text{ f} - 3.36 \text{ f} = \mathbf{39.08 \text{ fF}}$$



RESULT AND CONCLUSION

Simulated Value	Specifications
$A_v = 40.01 \text{ v/v}$	$A_v = 40 \text{ v/v}$
$BW = 25.06 \text{ MHz}$	$BW = 25 \text{ MHz}$
$GBW = 1.002 \text{ GHz}$	$GBW = 1 \text{ GHz}$
$R_{out} = 149.327 \text{ K}\Omega$	$R_{out} = 150 \text{ K}\Omega$
$I_d = 26.73 \text{ }\mu\text{A}$	$I_d = 26.6 \text{ }\mu\text{A}$
$V_{out(dc)} = 0.773 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$

SPICE ERROR LOG FILE

--- Transfer Function ---


Transfer_function:	-40.0109	transfer
vin#Input_impedance:	1e+020	impedance
output_impedance_at_V(vout):	149327	impedance

Semiconductor Device Operating Points:


--- BSIM3 MOSFETS ---

Name:	m2	m1
Model:	pch	nch
Id:	-2.67e-05	2.67e-05
Vgs:	-7.13e-01	6.58e-01
Vds:	-1.03e+00	7.74e-01
Vbs:	0.00e+00	0.00e+00
Vth:	-4.48e-01	4.59e-01
Vdsat:	-2.19e-01	1.52e-01
Gm:	1.87e-04	2.68e-04
Gds:	3.21e-06	3.49e-06
Gmb	5.86e-05	7.00e-05
Cbd:	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00
Cgsov:	2.38e-15	9.57e-16
Cgdov:	2.38e-15	9.57e-16
Cgbov:	2.98e-19	3.28e-19
dQgdVgb:	1.24e-14	6.48e-15
dQgdVdb:	-2.38e-15	-9.32e-16
dQgdVsb:	-9.67e-15	-5.23e-15
dQddVgb:	-2.39e-15	-9.63e-16
dQddVdb:	2.39e-15	9.60e-16
dQddVsb:	4.60e-18	4.49e-18
dQbdVgb:	-1.61e-15	-9.88e-16
dQbdVdb:	-5.20e-19	1.92e-18
dQbdVsb:	-7.20e-16	-4.05e-16

UNIT DEVICES

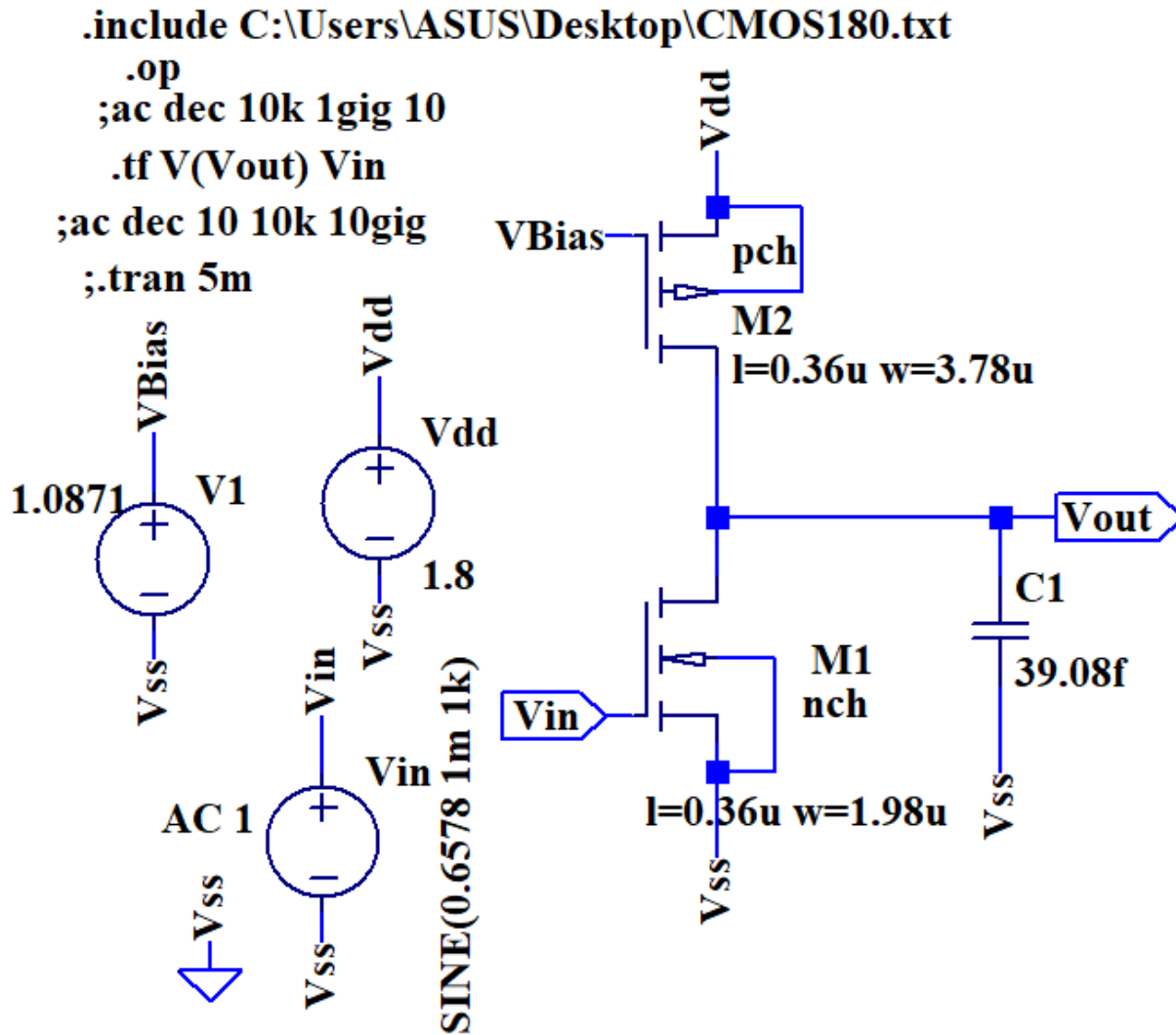

TRANSIENT ANALYSIS

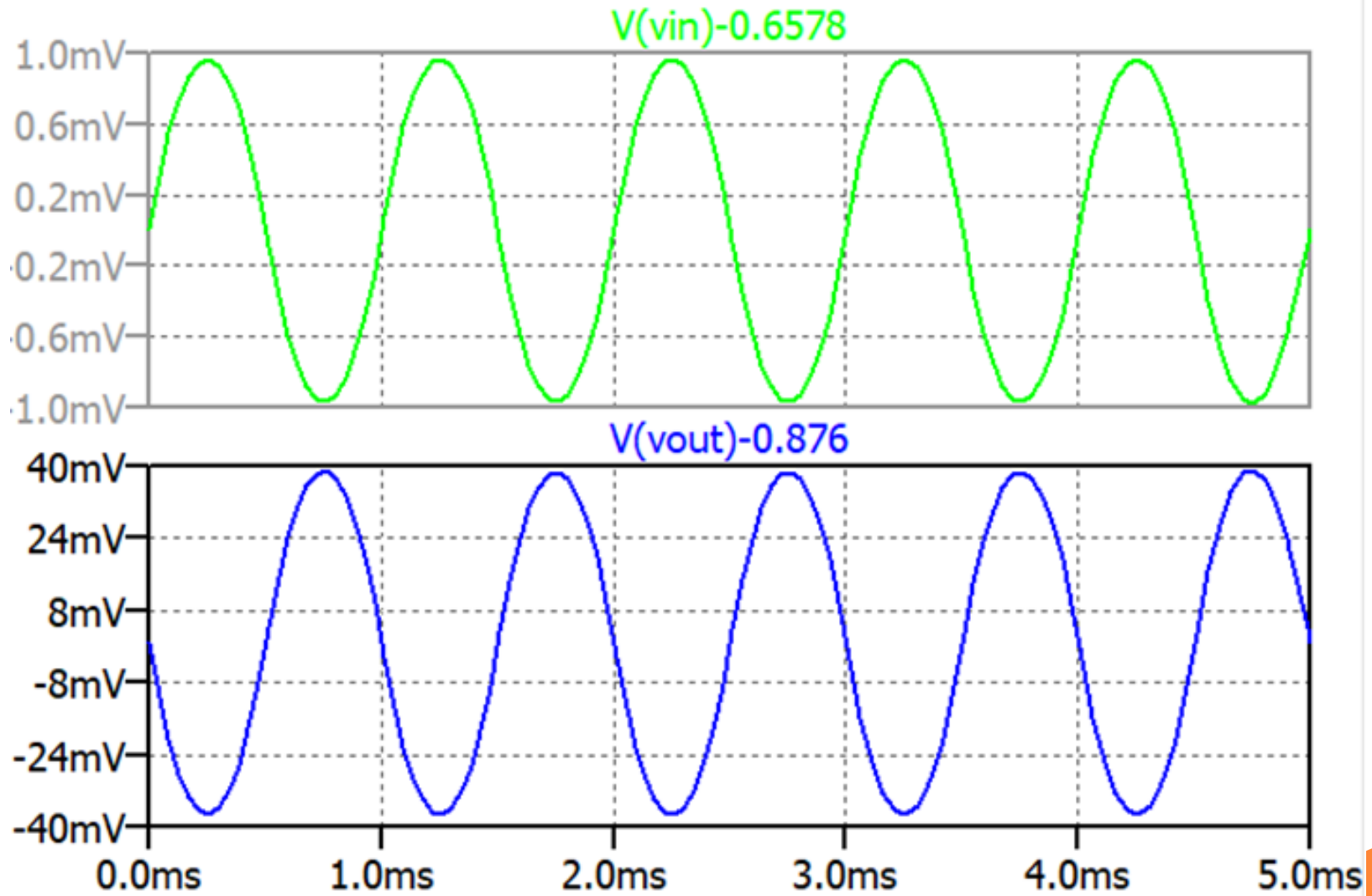


$V_{in}(p-p)=2 \text{ mV}$

$V_{out}=78.88 \text{ mV}$

Gain=39.44

FREQUENCY

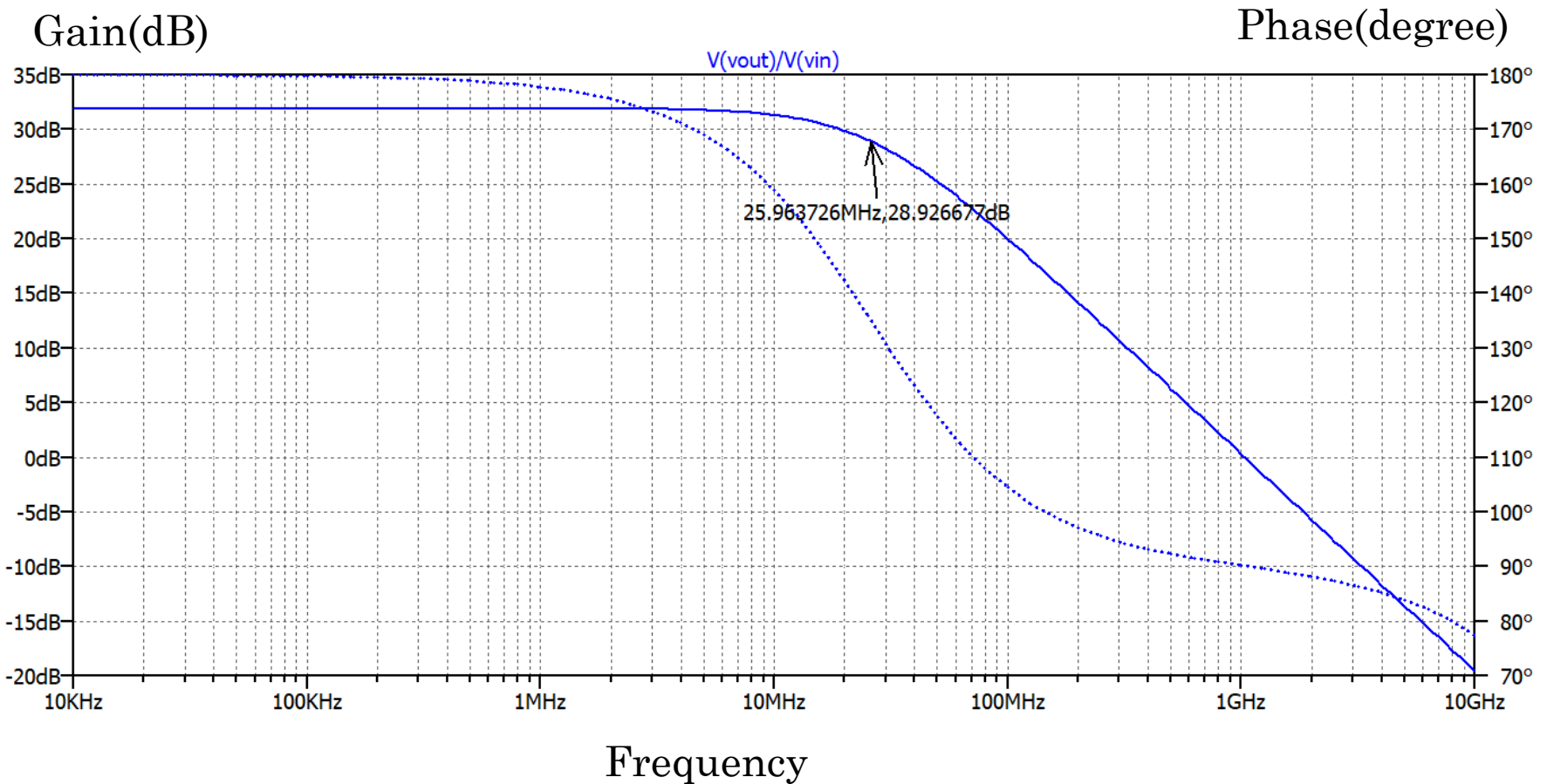



BW=25.96 MHz



DIFFERENTIAL PAIR

Using two Common Source Amplifier
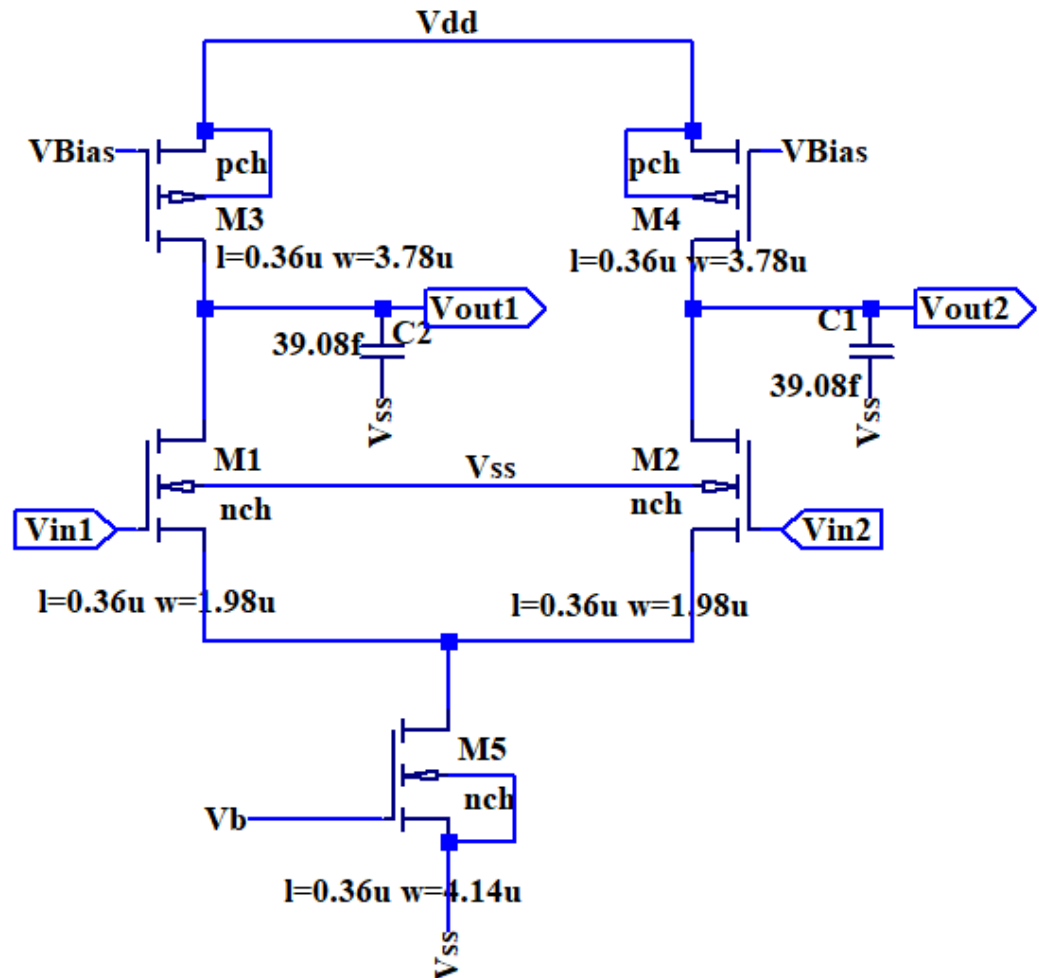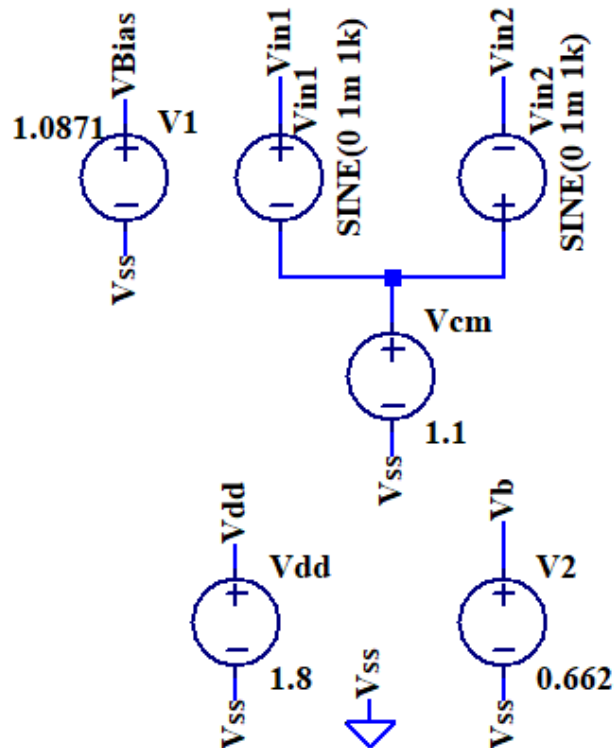
```
.include C:\Users\ASUS\Desktop\CMOS180.txt
.op
;ac dec 10k 1gig 10
.tf V(Vout1,Vout2) (Vin1,Vin2)
;ac dec 10 10k 10gig
;tran 5m
```



CALCULATION FOR CURRENT SOURCE

$$I_d = 54.96 \mu A$$


$$g_m/I_d = 10 \dots (\text{Choose})$$

$$V_{gs} = V_b = 0.662$$

$$I_d/w = 13.41$$


$$W_5 = 4.09 \mu m$$
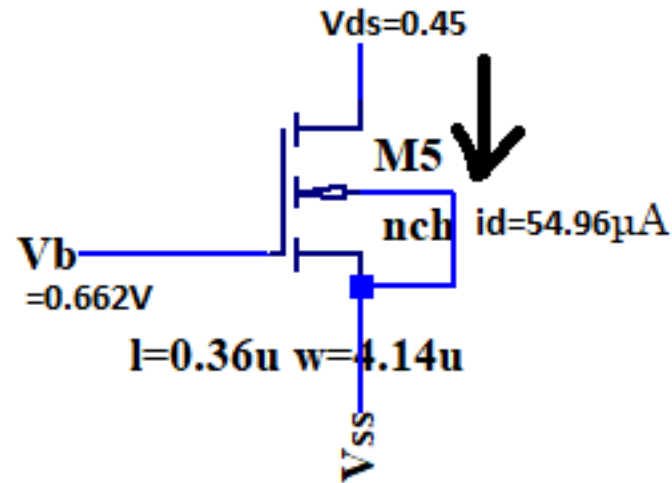
$$W_5 = 4.14 \mu m \dots \text{for unit device}$$




RESULT AND CONCLUSION

Simulated Value	Specifications
$A_v = 36.18 \text{ v/v}$	$A_v = 40 \text{ v/v}$
$BW = 28.66 \text{ MHz}$	$BW = 25 \text{ MHz}$
$GBW = 1.03 \text{ GHz}$	$GBW = 1 \text{ GHz}$
$R_{out} = 263.492 \text{ K}\Omega$	
$I_{ss} = 54.46 \text{ }\mu\text{A}$	$I_{ss} = 54.96 \text{ }\mu\text{A}$
$V_{out(dc)} = 0.949 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$

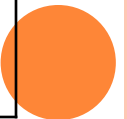


TRANSIENT ANALYSIS

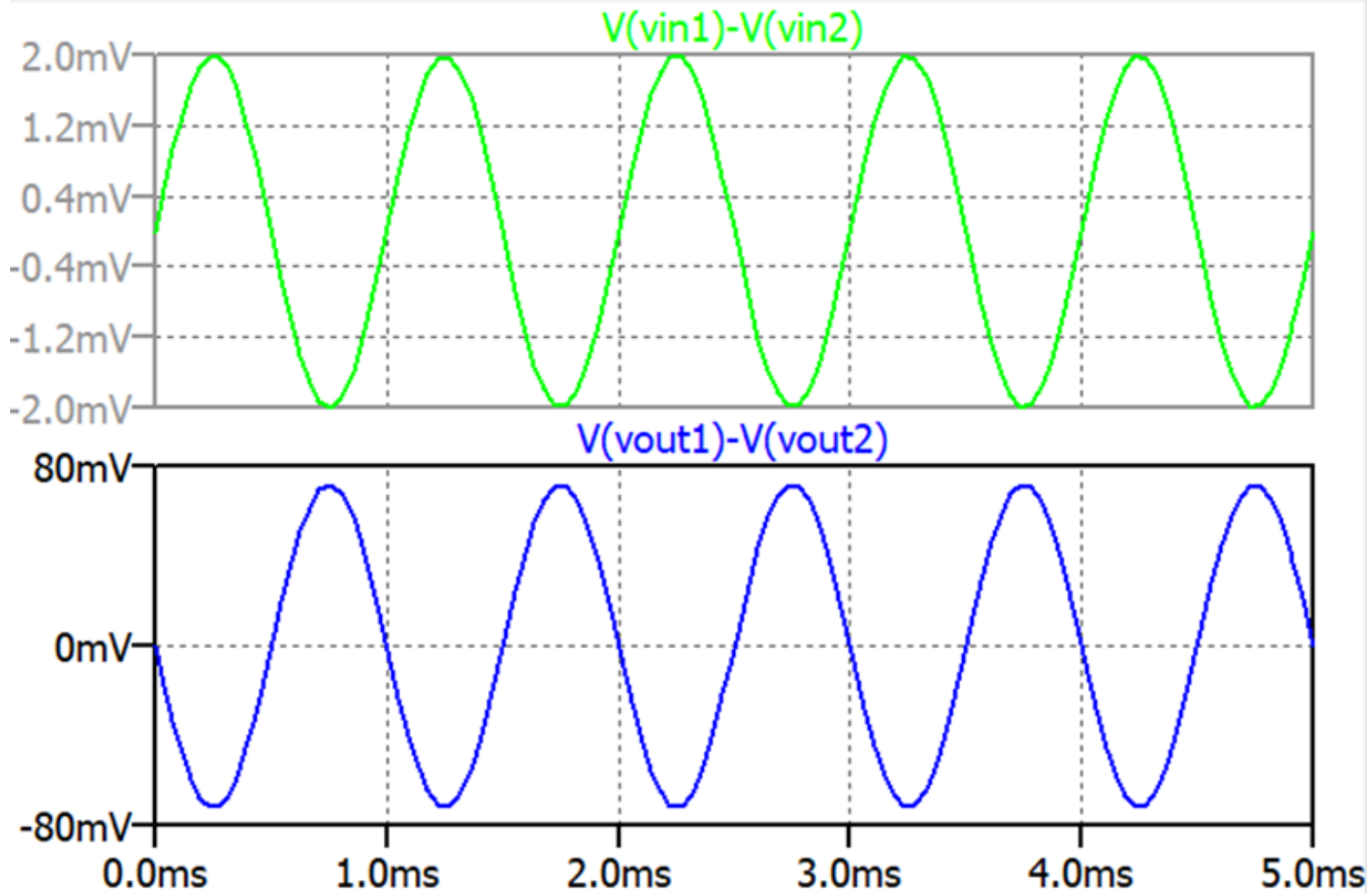

$V_{\text{in1}} - V_{\text{in2}}(\text{pp}) = 4 \text{ mV}$ $V_{\text{out1}} - V_{\text{out2}}(\text{pp}) = 144.56 \text{ mV}$ Gain = 36.14



FREQUENCY RESPONSE

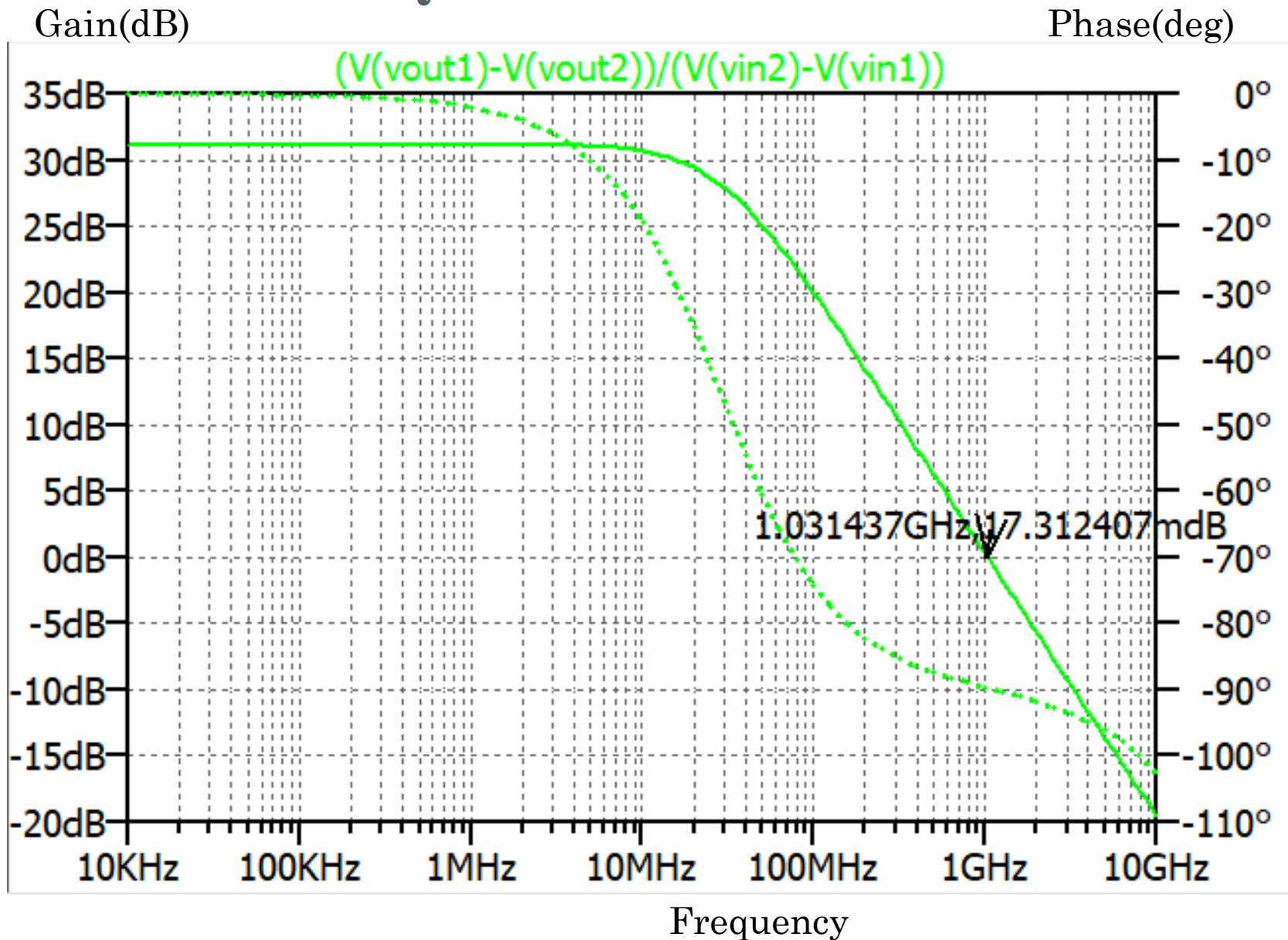

COMMON SOURCE AMPLIFIER

Specs:

$A_v=40$

$R_{out}=93\text{ K}\Omega$

Formula Used

$$A_v = g_m \cdot R_{out}$$

$$W = \frac{I_D}{I_D/W}$$

$$R_{out} = R_{o1} \parallel R_{o3}$$

$$g_{ds} = \frac{1}{r_o}$$

○ $g_m = 0.43\text{ mS}$

○ $g_m/I_D = 12$

○ $I_D = 35.8\text{ }\mu\text{A}$

○ $R_{o1} = 165\text{ K}\Omega$

○ $g_{ds3} = 4.69\text{ }\mu\text{S}$

○ $(I_D/g_{ds})_3 = 7.63$

○ $g_m/I_D = 6.315$

○ $W_3 = 3.91\text{ }\mu\text{m}$

$$g_m/g_{ds} = 70.92$$

$$g_{ds} = 6.06\text{ }\mu\text{S}$$

$$R_{o3} = 213.125\text{ K}\Omega$$

$$I_D/W = 9.896$$

$$W_1 = 3.61\text{ }\mu\text{m}$$


$$I_D/W = 9.133$$



SIMULATION

.include C:\Users\ASUS\Desktop\CMOS180.txt

.tf V(Vout) Vin

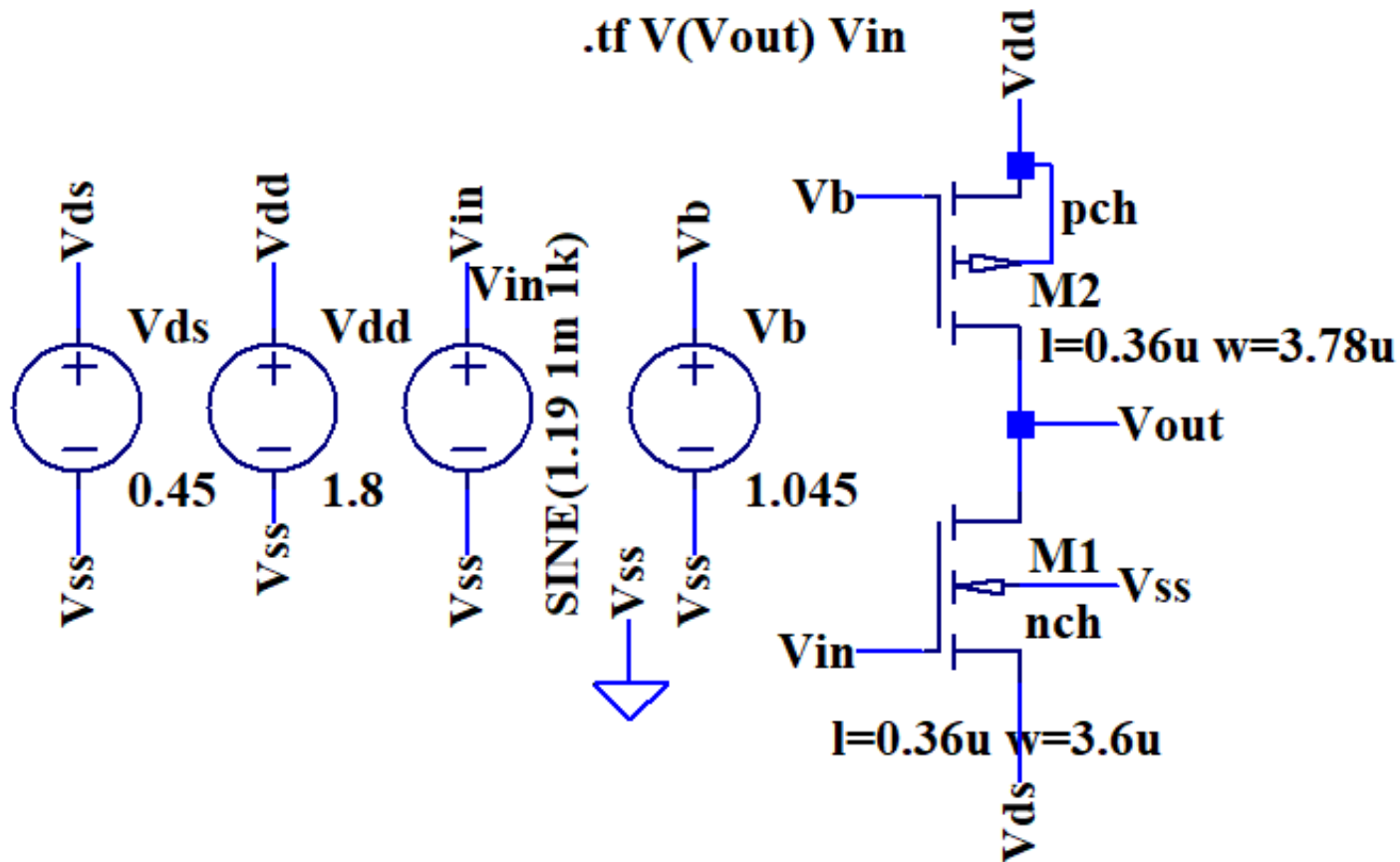


RESULTS

Simulated Value	Specifications
$A_v = 40.15 \text{ v/v}$	$A_v = 40 \text{ v/v}$
$R_{out} = 95.632 \text{ K}\Omega$	$R_{out} = 93 \text{ K}\Omega$
$I_d = 35.18 \text{ }\mu\text{A}$	$I_d = 35.8 \text{ }\mu\text{A}$
$V_{out(dc)} = 1.07 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$




OP-AMP (STAGE-1)

Using Common Source Amplifier

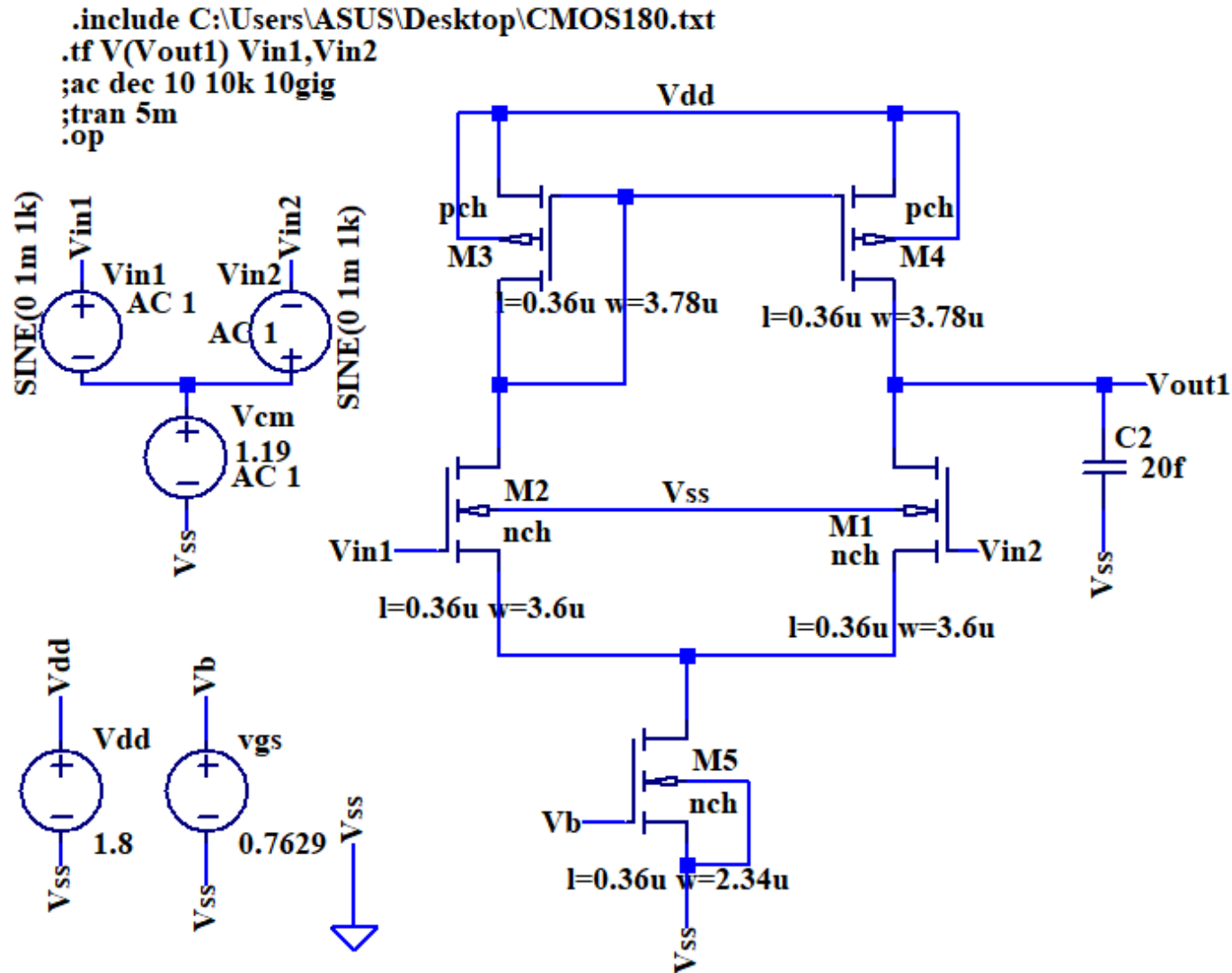


RESULT


Simulated Value	Specifications
$A_v = 39.8092 \text{ v/v}$	$A_v = 40 \text{ v/v}$
$BW = 28.66 \text{ MHz}$	$BW = 25 \text{ MHz}$
$GBW = 1.03 \text{ GHz}$	$GBW = 1 \text{ GHz}$
$R_{out} = 97.259 \text{ K}\Omega$	$R_{out} = 93 \text{ K}\Omega$
$I_{ss} = 70.3 \text{ }\mu\text{A}$	$I_{ss} = 71.6 \text{ }\mu\text{A}$
$V_{out(dc)} = 1.04 \text{ V}$	$V_{out(dc)} = 1.15 \text{ V}$



FREQUENCY ANALYSIS

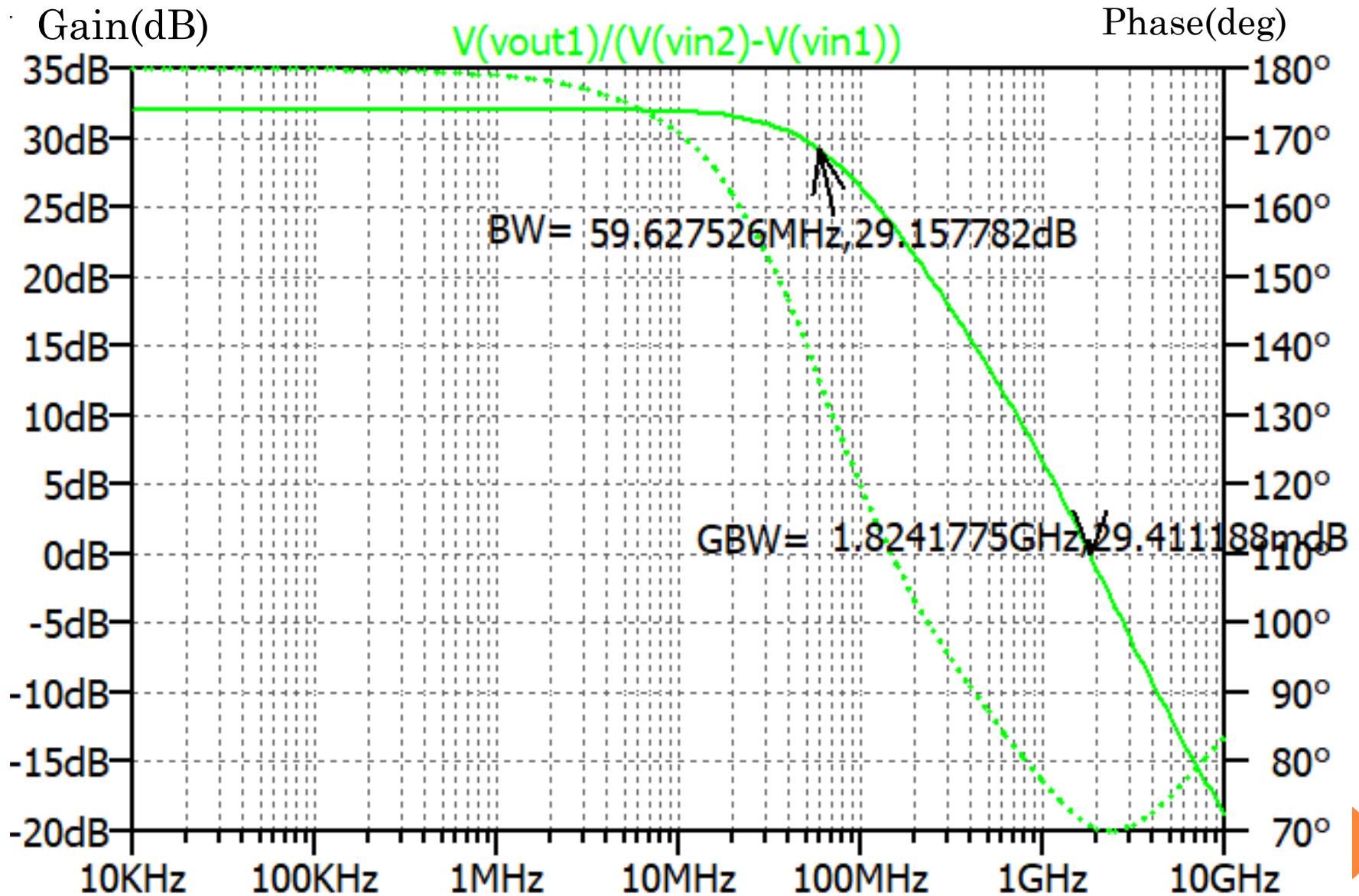

TRANSIENT ANALYSIS

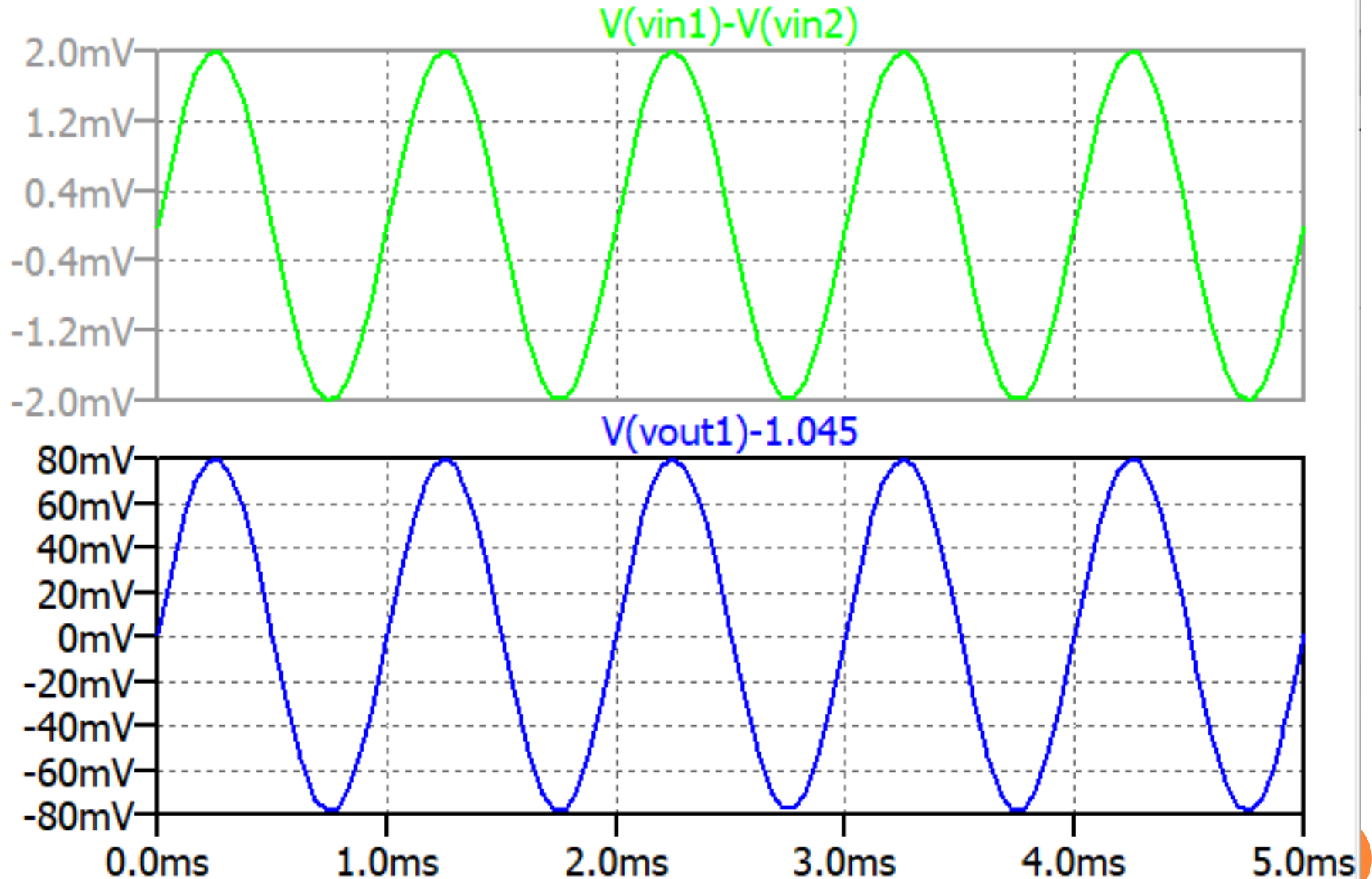

$V_{\text{in1}}-V_{\text{in2}}(\text{pp})=4 \text{ mV}$ $V_{\text{out1}}(\text{pp})=158.68 \text{ mV}$ $\text{Gain}=39.67$

COMMON SOURCE AMPLIFIER

For Second Stage op-amp

Specs:

$$A_v = 28$$

$$g_{m2} = 8 \times 0.432 \text{ mS} = 3.384 \text{ mS}$$

$$R_{out2} = 8 \text{ K}\Omega$$

- $V_{gs1} = 780 \text{ mV}$

- $g_m/i_d = 5.466$ $i_d/w = 11.9$ from chart

- $g_m/g_{ds} = 46.96$ from chart

- $I_d = 619 \text{ }\mu\text{A}$

- $W_6 = 52 \text{ }\mu\text{m}$

- $g_{ds6} = 72.06 \text{ }\mu\text{S}$ $R_{o6} = 13.87 \text{ K}\Omega$

- $R_{o7} = 18.9 \text{ K}\Omega$ $g_{ds7} = 52.9 \text{ }\mu\text{S}$



- $(I_d/g_{ds})_7 = 11.7$
- $g_m/i_d = 6.24$ $i_d/w = 31.05$
- $W_7 = 19.9 \mu\text{m}$ **$W_7 = 15.84 \mu\text{m}$ in Simulation**
- $V_{gs7} = 0.7629 \text{ V}$



SIMULATION


```
.include C:\Users\ASUS\Desktop\CMOS180.txt
```

```
.tf V(Vout) Vin
```

```
;ac dec 10 10k 10gig
```

```
;tran 5m
```

```
.op
```

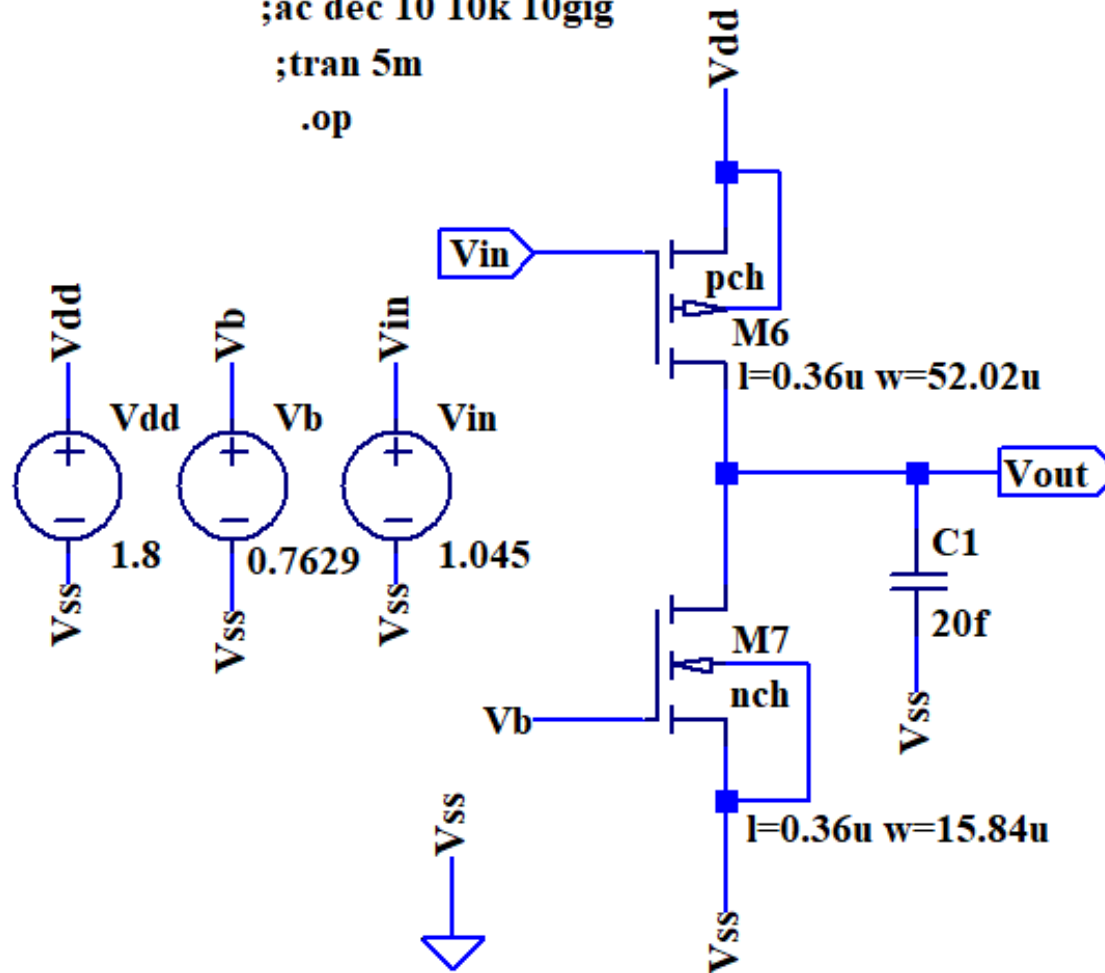


RESULT


Simulated Value	Specifications
$A_v = 28.34 \text{ v/v}$	$A_v = 28 \text{ v/v}$
$BW = 256.9 \text{ MHz}$	
$GBW = 9.24 \text{ GHz}$	
$R_{out} = 9.6 \text{ K}\Omega$	$R_{out} = 8 \text{ K}\Omega$
$I_{B2} = 494 \text{ }\mu\text{A}$	$I_{B2} = 619 \text{ }\mu\text{A}$
$V_{out(dc)} = 0.998 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$



FREQUENCY RESPONSE

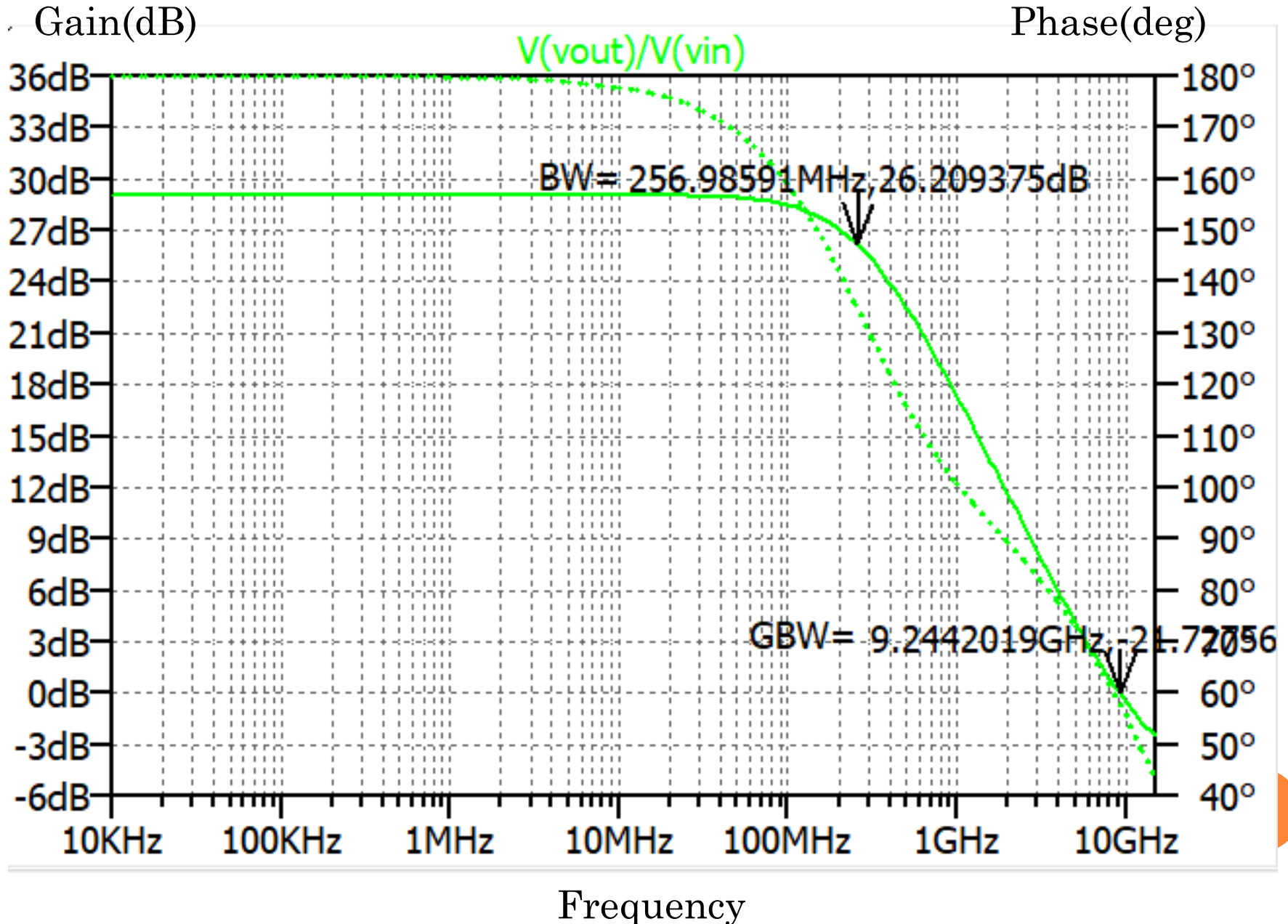

TRANSIENT ANALYSIS

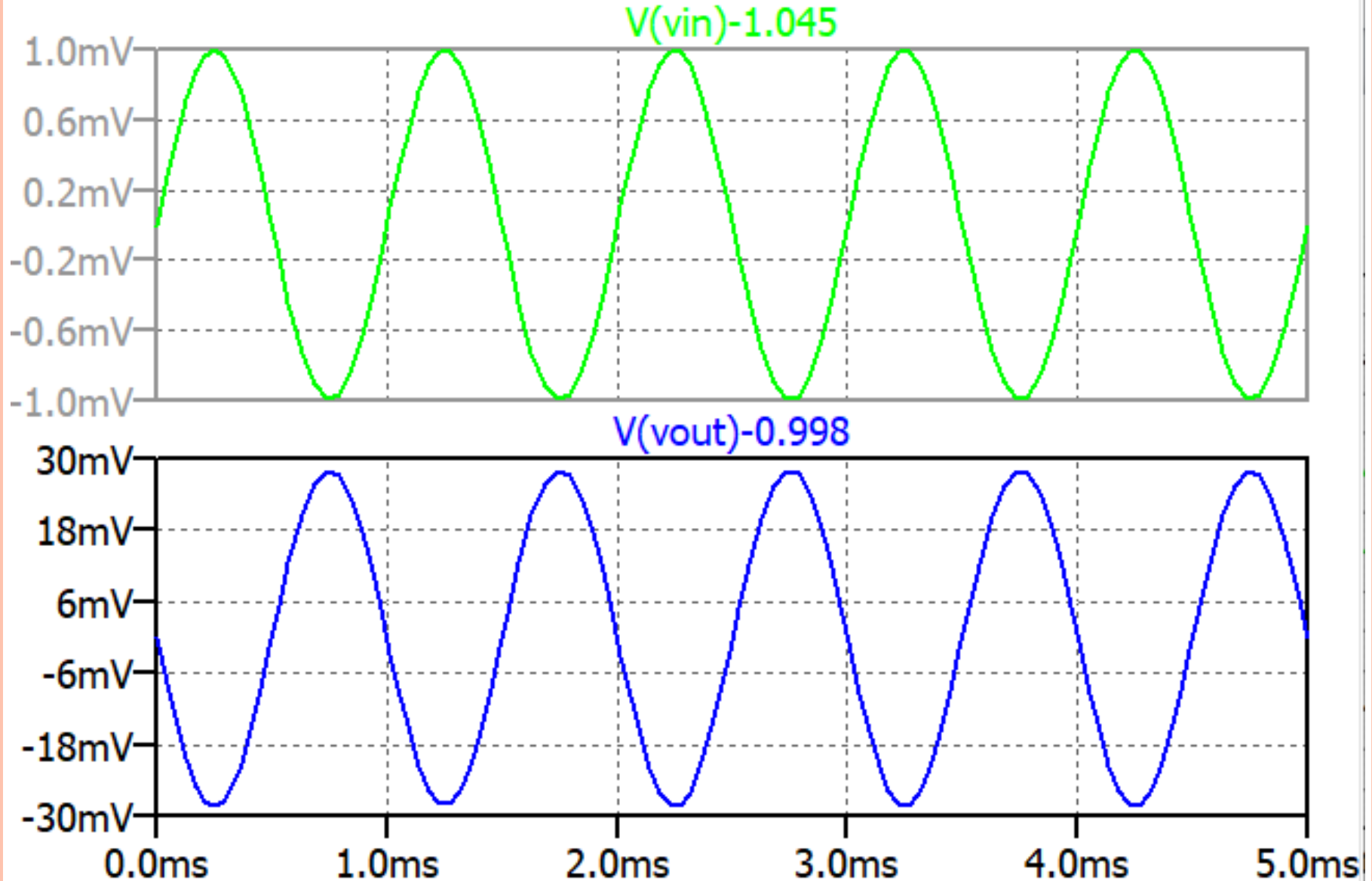

$V_{in(pp)}=2 \text{ mV}$ $V_{out(pp)}=56.63 \text{ mV}$ Gain=28.315

PROJECT: DESIGNING OF TWO STAGE OPERATIONAL AMPLIFIER


Specification

Gain(A_v)	≥ 1000 (60dB)
GBW	1GHz
Phase Margin	≥ 50
Load Capacitance	20 fF




PROJECT: TWO STAGE OP-AMP

Combining Stage-1 and Stage-2

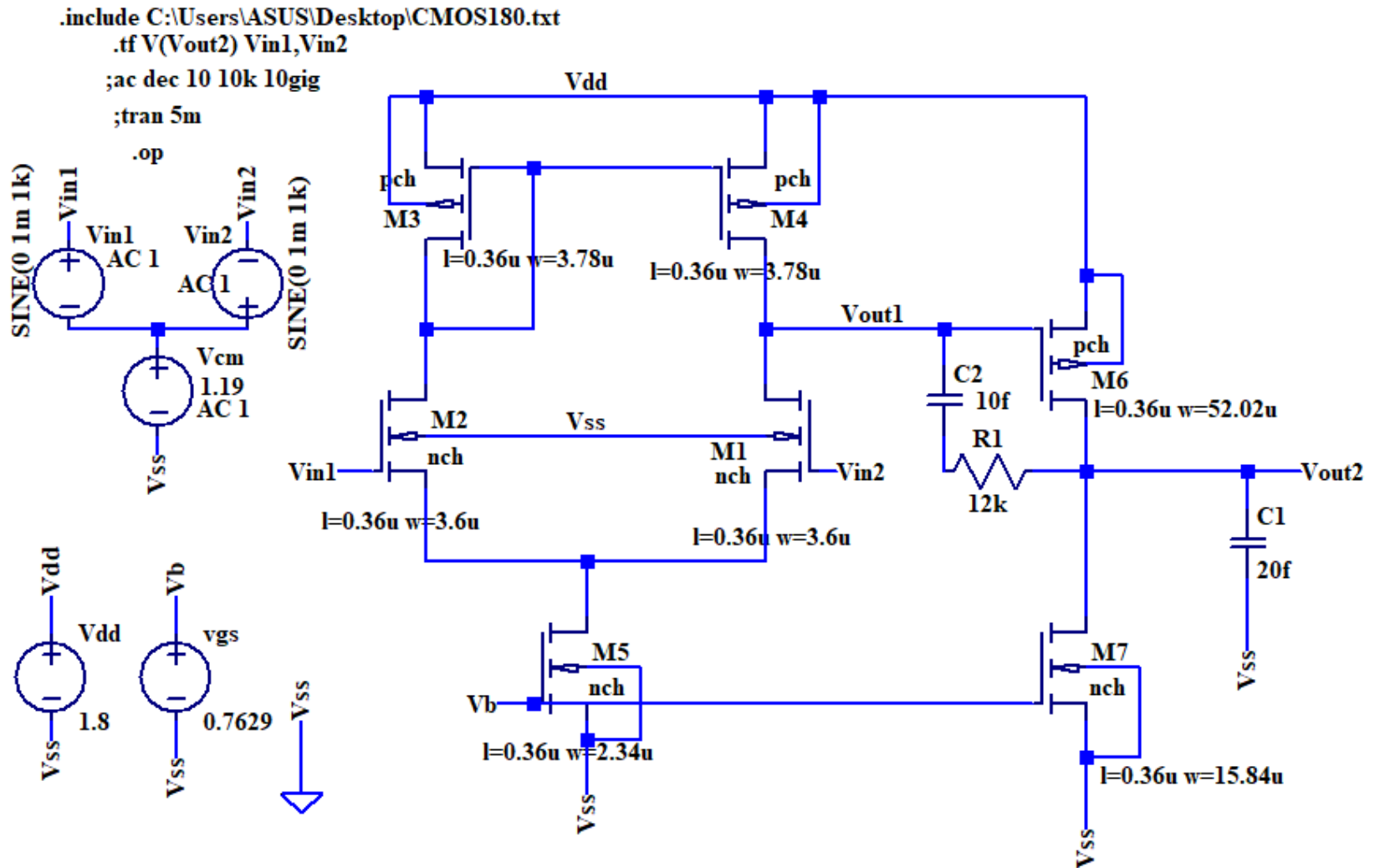

CAPACITOR

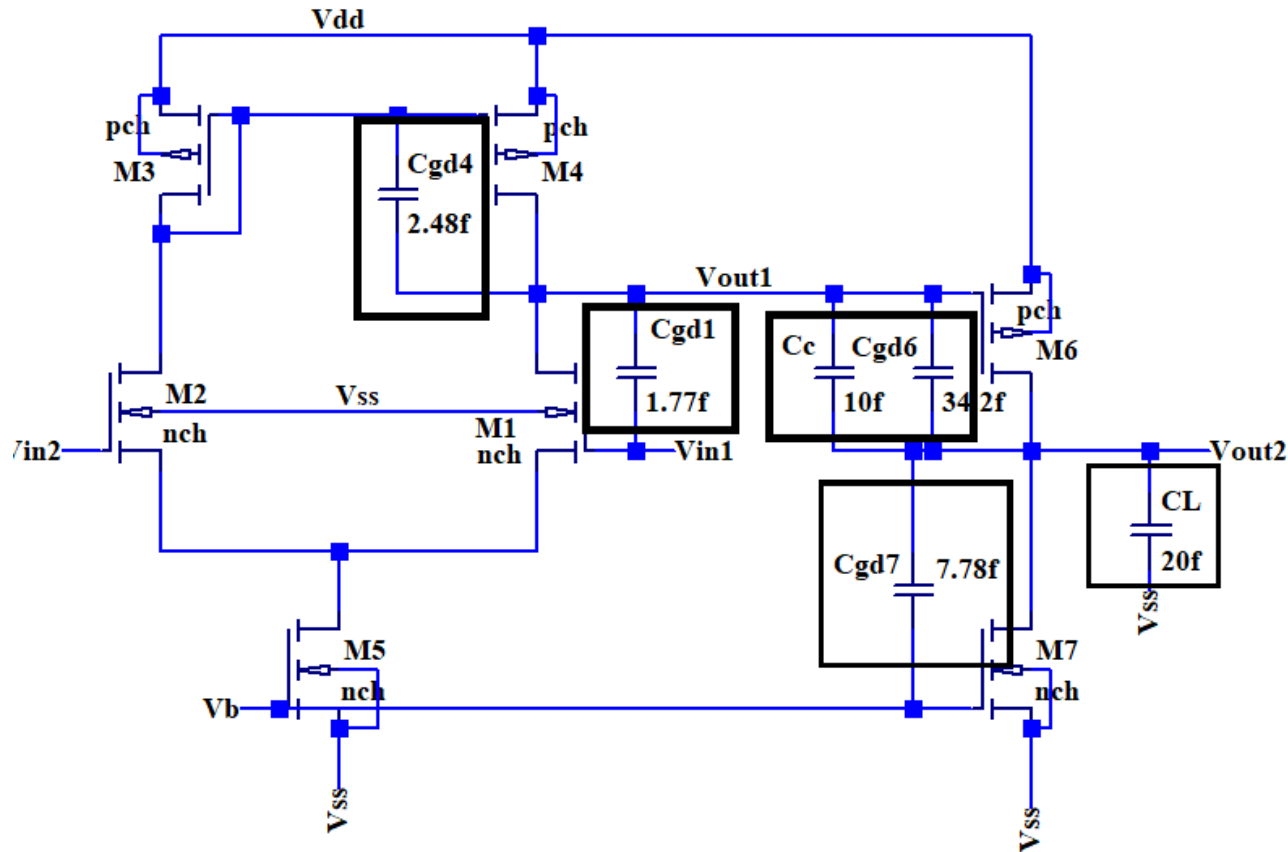

$C1 = \text{Capacitance at Node}(V_{out1}) = C_{gd4} + C_{gd1} + \{ (C_{gd6} + C_c) * (1 + A_{v2}) \}$

$C1 = 1.3 \text{ pF}$

$C2 = \text{Capacitance at Node}(V_{out2}) = C_L + C_{gd7} + \{ (C_{gd6} + C_c) * (1 + \frac{1}{A_{v2}}) \}$

$C2 = 73.52 \text{ fF}$



POLE AND ZERO

- Dominant Pole

- $F_{p1} = \frac{1}{2\pi \cdot R_{out1} \cdot C1}$

- $F_{p1} = 1.2 \text{ MHz}$ where $R_{out1} = 97.25 \text{ K}\Omega$

- $F_{p2} = \text{Beyond } 1\text{GHz}$

- $S_z = \frac{1}{C_c \left(\frac{1}{G_{m6}} - R_z \right)}$

- $F_z = -1.36\text{GHz}$ where $R_z = 12\text{k}$, $G_{m2} = 2.95\text{mS}$



FREQUENCY COMPENSATION

- $C_c = 10 \text{ fF}$ (generally $C_c = (0.3 - 0.5) * C_L$)
- $R_z = 12 \text{ K}\Omega$ (generally $R_z = 1 / G_{m2}$)
- But we have taken $12 \text{ K}\Omega$ for achieving Phase Margin of 45° .



RESULT

Simulated Value	Specifications
$A_v = 1139 \text{ v/v}$	$A_v \geq 1000 \text{ v/v}$
$BW = 1.12 \text{ MHz}$	$BW = 1 \text{ MHz}$
$GBW = 1.02 \text{ GHz}$	$GBW = 1 \text{ GHz}$
$R_{out} = 9.68 \text{ K}\Omega$	$R_{out} = 8 \text{ K}\Omega$
$V_{out(dc)} = 0.97 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$
$I_{B1} = 70.3 \text{ }\mu\text{A}$, $I_{B2} = 493.24 \text{ }\mu\text{A}$ Total Current = $563.54 \text{ }\mu\text{A}$ $V_{dd} = 1.8$ Power Dissipation = 1.01 mW	- - - -
Phase Margin = 45°	Phase Margin = 50°
Gain Margin = 16.5 dB	-
$C_L = 20 \text{ fF}$	$C_L = 20 \text{ fF}$

TABLE

Stage 1	Stage 2
$L=0.36\mu\text{m}$	$L=0.36\mu\text{m}$
$W_{1,2} = 3.6\mu\text{m}$ $\frac{W}{L} = 10$	$W_6=52.02\mu\text{m}$ $\frac{W}{L} = 144.5$
$gm_{1,2} = 0.419 \text{ mS}$	$gm_6 = 2.59 \text{ mS}$
$W_{3,4} = 3.78\mu\text{m}$ $\frac{W}{L} = 10.5$	$W_7= 15.84 \mu\text{m}$ $\frac{W}{L} = 44$
$gm_{3,4} = 0.21 \text{ mS}$	$gm_7 = 3.05 \text{ mS}$



SPICE ERROR LOG FILE

Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---


Name:	m6	m3	m4	m7	m5	m2	m1
Model:	pch	pch	pch	nch	nch	nch	nch
Id:	-4.93e-04	-3.52e-05	-3.52e-05	4.93e-04	7.03e-05	3.52e-05	3.52e-05
Vgs:	-7.54e-01	-7.54e-01	-7.54e-01	7.63e-01	7.63e-01	7.40e-01	7.40e-01
Vds:	-8.26e-01	-7.54e-01	-7.54e-01	9.74e-01	4.50e-01	5.96e-01	5.96e-01
Vbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	-4.50e-01	-4.50e-01
Vth:	-4.50e-01	-4.48e-01	-4.48e-01	4.58e-01	4.62e-01	5.82e-01	5.82e-01
Vdsat:	-2.55e-01	-2.50e-01	-2.50e-01	2.19e-01	2.15e-01	1.38e-01	1.38e-01
Gm:	2.95e-03	2.11e-04	2.11e-04	3.05e-03	4.40e-04	4.19e-04	4.19e-04
Gds:	6.24e-05	4.69e-06	4.69e-06	4.09e-05	1.09e-05	5.73e-06	5.73e-06
Gmb:	9.53e-04	6.66e-05	6.66e-05	7.91e-04	1.13e-04	9.52e-05	9.52e-05
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	3.42e-14	2.48e-15	2.48e-15	7.78e-15	1.15e-15	1.77e-15	1.77e-15
Cgdov:	3.42e-14	2.48e-15	2.48e-15	7.78e-15	1.15e-15	1.77e-15	1.77e-15
Cgbov:	2.98e-19	2.98e-19	2.98e-19	3.28e-19	3.28e-19	3.28e-19	3.28e-19
dQgdVgb:	1.78e-13	1.30e-14	1.30e-14	5.26e-14	7.80e-15	1.18e-14	1.18e-14
dQgdVdb:	-3.42e-14	-2.48e-15	-2.48e-15	-7.58e-15	-1.13e-15	-1.72e-15	-1.72e-15
dQgdVsb:	-1.38e-13	-1.01e-14	-1.01e-14	-4.27e-14	-6.32e-15	-9.53e-15	-9.53e-15
dQddVgb:	-3.43e-14	-2.50e-15	-2.50e-15	-7.81e-15	-1.19e-15	-1.78e-15	-1.78e-15
dQddVdb:	3.43e-14	2.49e-15	2.49e-15	7.79e-15	1.18e-15	1.78e-15	1.78e-15
dQddVsb:	1.04e-16	8.68e-18	8.68e-18	2.36e-17	1.14e-17	1.33e-17	1.33e-17
dQbdVgb:	-2.25e-14	-1.67e-15	-1.67e-15	-7.92e-15	-1.17e-15	-1.67e-15	-1.67e-15
dQbdVdb:	-2.52e-17	-2.70e-18	-2.70e-18	1.63e-17	-9.51e-18	7.38e-19	7.38e-19
dQbdVsb:	-1.10e-14	-7.45e-16	-7.45e-16	-3.25e-15	-4.67e-16	-4.71e-16	-4.71e-16

--- Transfer Function ---

Transfer_function:	-1139.14	transfer	
vin1#Input_impedance:	1e+020	impedance	
output_impedance_at_V(vout2):		9688.45	impedance




FREQUENCY RESPONSE

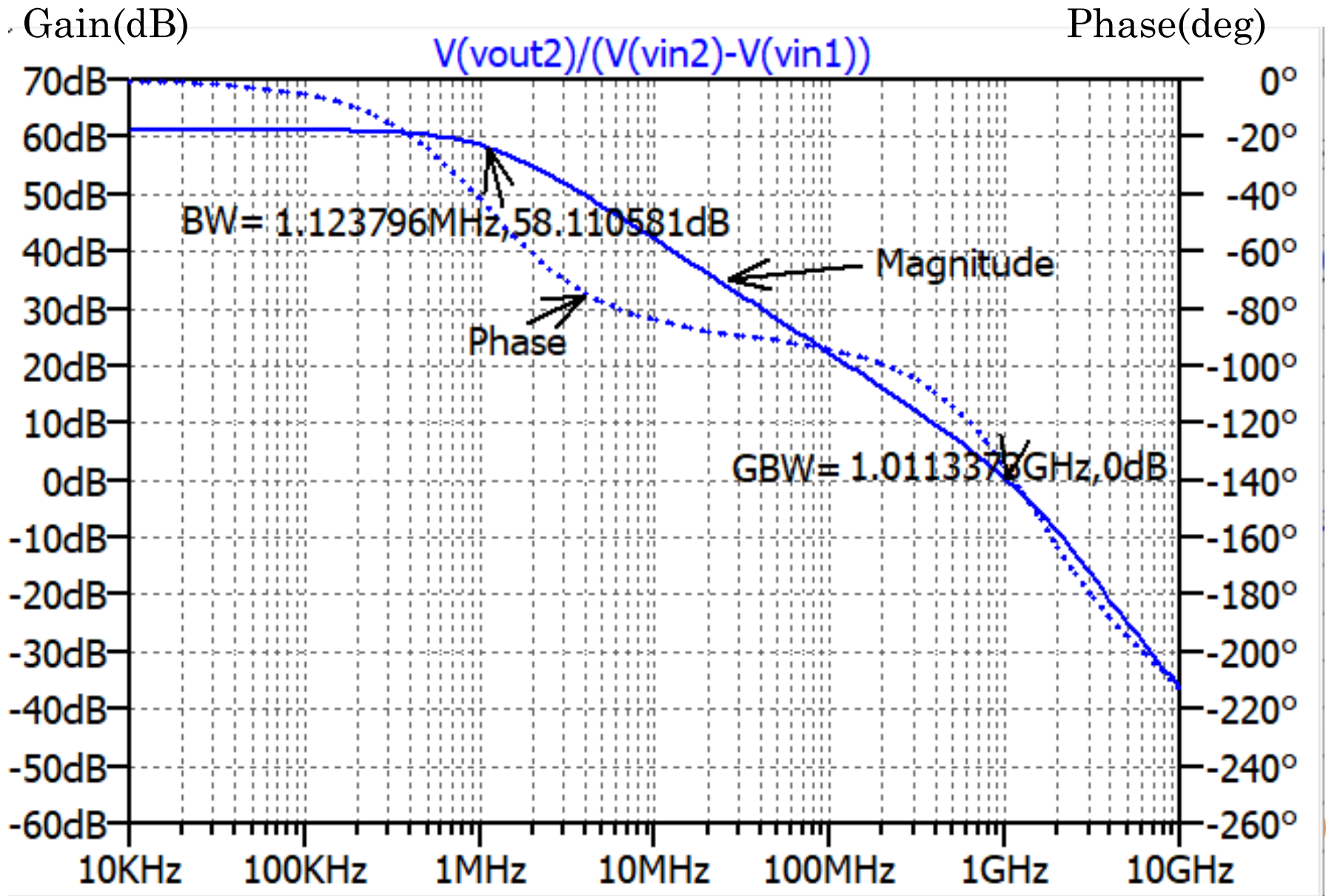

Frequency

TRANSIENT ANALYSIS

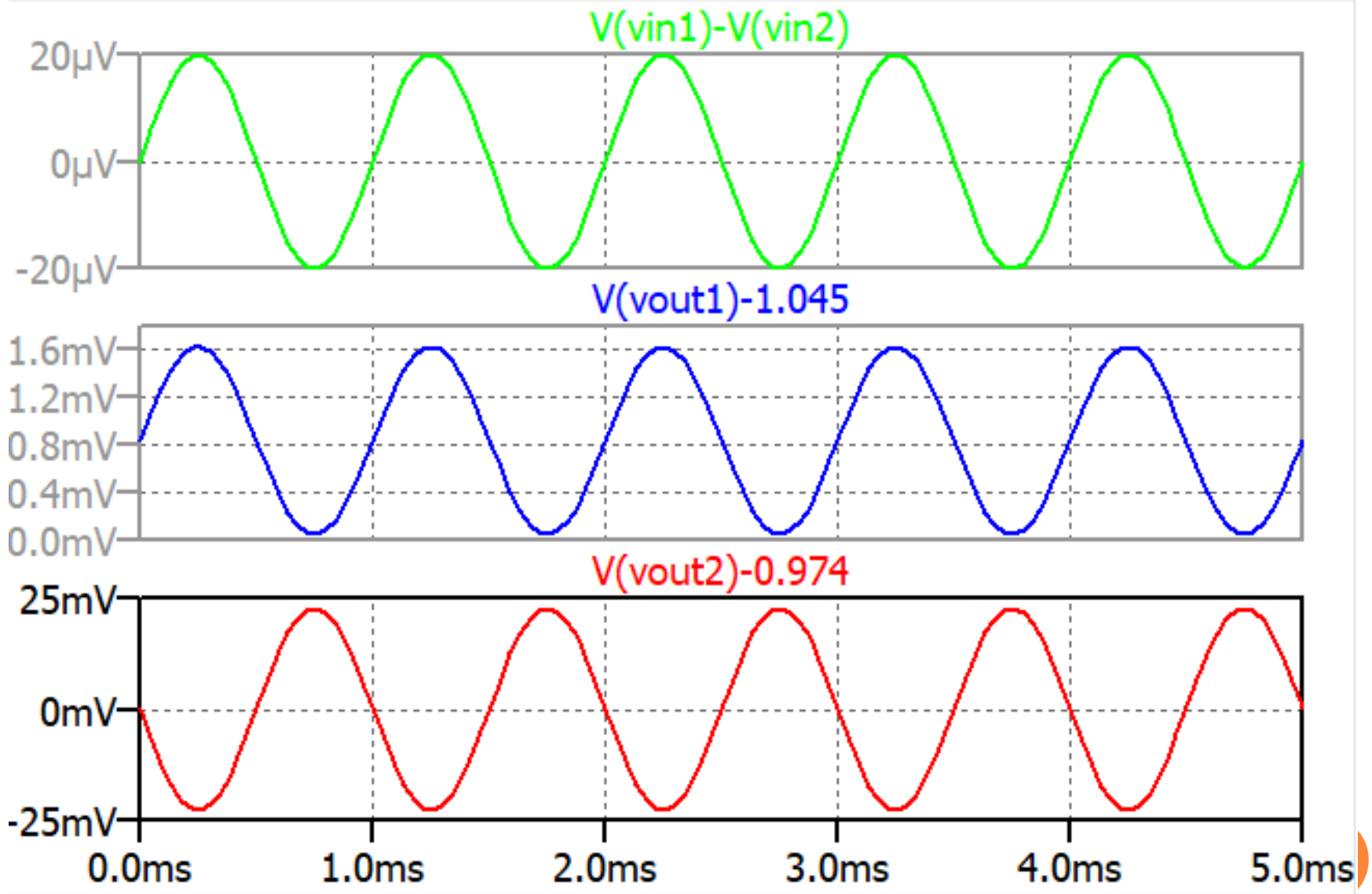

$V_{\text{in1}}-V_{\text{in2}}(\text{pp})=40\mu\text{V}$ $V_{\text{out2}}(\text{pp})=45.54\text{mV}$ $\text{Gain}=1138.5$

LEARN IN THIS INTERNSHIP

- Learn gmid methodology for designing Amplifier.
- How to Extract different charts used in gmid method
- Designed using ADT Toolbox
- Able to Design Amplifier with given Specification
- Completed project: Design of two Stage op-amp with gain bandwidth product of 1Ghz.



REFERENCES

- IEEE.ORG
- The Design of Two-Stage Miller Op-Amp: The Final Verdict! | Dr. Hesham Omran, Youtube Link: https://youtu.be/PT31xAEd_v4



Special Thanks to:

- Prof Syed Atiqur Rahman Sir
- Prof Mohammad Jawaid Siddiqui Sir
 - Dr Saif Abrar Sir
 - Mudassir Sir
 - Shamsul Haque Sir
 - Mohd Kashif Sir
 - Ayush Sharma
 - Afzal Malik
 - Mohsin Hussain
- &
- My Parents



Thank you

